

# Digital Logic Design + Computer Architecture

Sayandeep Saha

Assistant Professor  
Department of Computer  
Science and Engineering  
Indian Institute of Technology  
Bombay






# Sequential Circuits



# A Circuit that Remembers


- How do you remember things?
  - Memory
- Can we design a circuit which remembers?
  - A formal way to model this capability is called a **state**
  - So we will be modelling circuits to create a **state**.

**Remember**

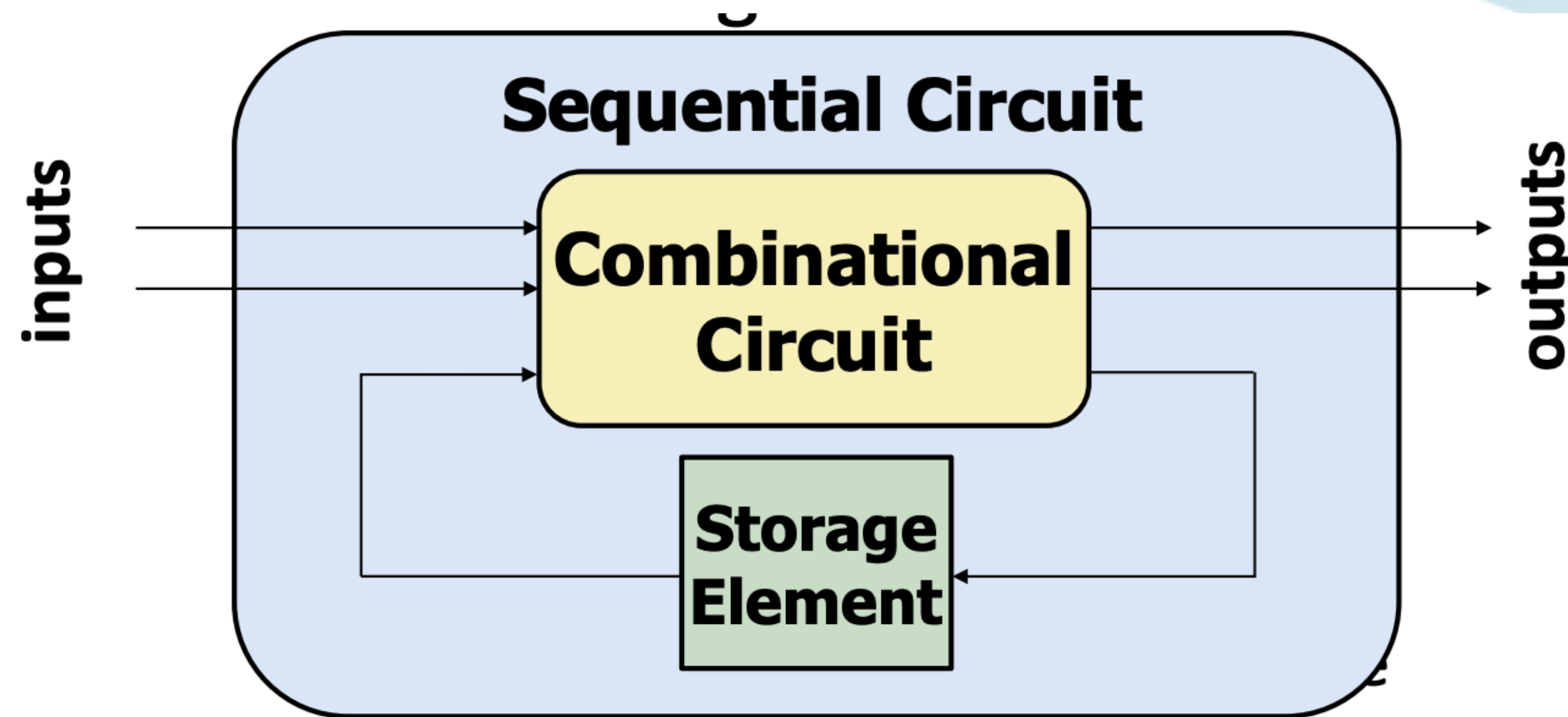
 
# A Circuit that Remembers

- **Every digital logic you see in real life is sequential**
  - Your processors — that you going to see in the rest of the course
  - Your washing machine — it remembers your setting and washes accordingly
  - Your elevator — it remembers which floors to stop
  - Your ATM machine — it remembers your choice and updates your account after despatching money



# Sequential Circuits and Finite State Machines


**Sequential circuit:** its outputs a function of external inputs as well as stored information (aka. State)

**Finite-state machine (FSM):** abstract model to describe the synchronous sequential machines. It has finite memory.

**Serial binary adder example:** block diagram, addition process, state table and state diagram


Let A denote the state of the adder at  $t_i$  if the carry 0 is generated at  $t_{i-1}$

 Let B denote the state of the adder at  $t_i$  if the carry 1 is generated at  $t_{i-1}$



$$\begin{array}{r}
 t_5 \ t_4 \ t_3 \ t_2 \ t_1 \\
 0 \ 1 \ 1 \ 0 \ 0 \ = \ X_1 \\
 + \ 0 \ 1 \ 1 \ 1 \ 0 \ = \ X_2 \\
 \hline
 1 \ 1 \ 0 \ 1 \ 0 \ = \ Z
 \end{array}$$

$PS$	$NS, z$			
	$x_1 x_2 = 00$	01	11	10
$A$	$A, 0$	$A, 1$	$B, 0$	$A, 1$
$B$	$A, 1$	$B, 0$	$B, 1$	$B, 0$

 

# Sequential Circuits and Finite State Machines

**Two states** capable of storing information regarding the **presence or absence of carry**:


**delay element** with input  $Y$  and output  $y$

- Two states:  $y = 0$  and  $y = 1$
- The capability of the device to store information is the result of the fact that it takes some time for the input signal  $Y$  to pass to the output  $y$ 
  - Compare with a combinational gate where the output changes almost immediately. In this device there is some well-defined time required before the input  $Y$  passes to the output  $y$ . **During that time-window, the old value stays!**
- Since the **present input value**  $Y$  of the delay element is equal to its **next output value**: the input value is referred to as the next state of the delay
  - $y(t+1)=Y(t)$


**Example:** assign state  $y = 0$  to state  $A$  of the adder and  $y = 1$  to  $B$

- The value of  $y$  at  $t_i$  corresponds to the value of the carry generated at  $t_{i-1}$
- Process of assigning the states of a physical device to the states of the serial adder: called **state assignment**
- Output value  $y$ : referred to as the **state variable**
- **Transition/output table** for the serial adder:

$y$	Next state $Y$				Output $z$			
	$x_1x_2$				$x_1x_2$			
	00	01	11	10	00	01	11	10
0	0	0	1	0	0	1	0	1
1	0	1	1	1	1	0	1	0

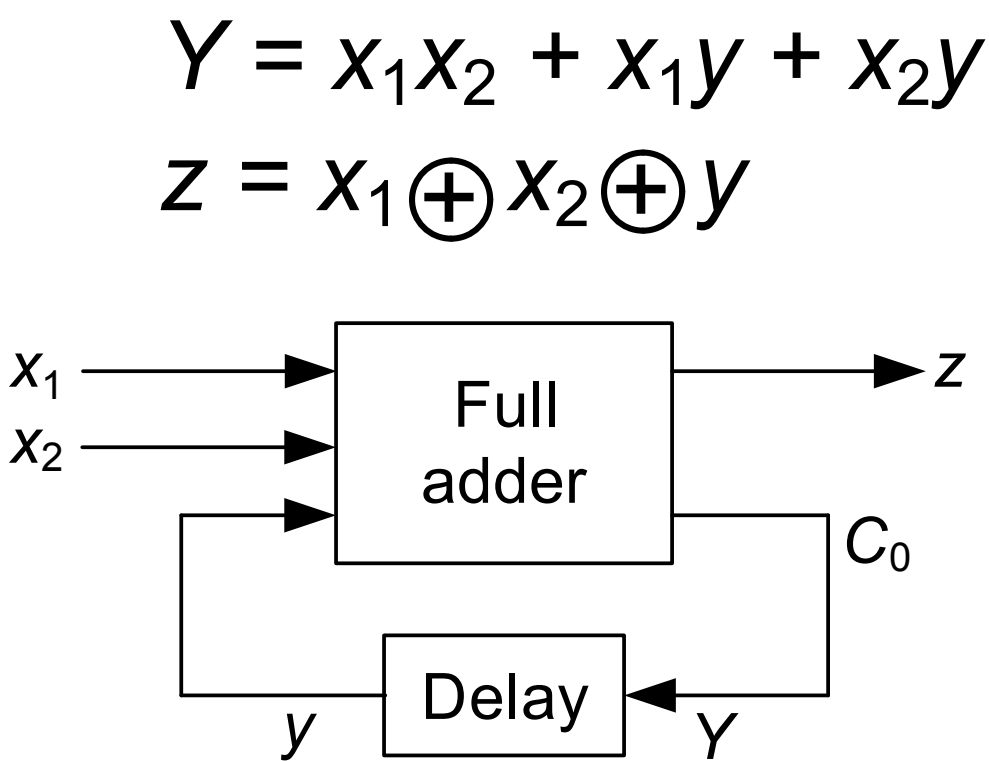
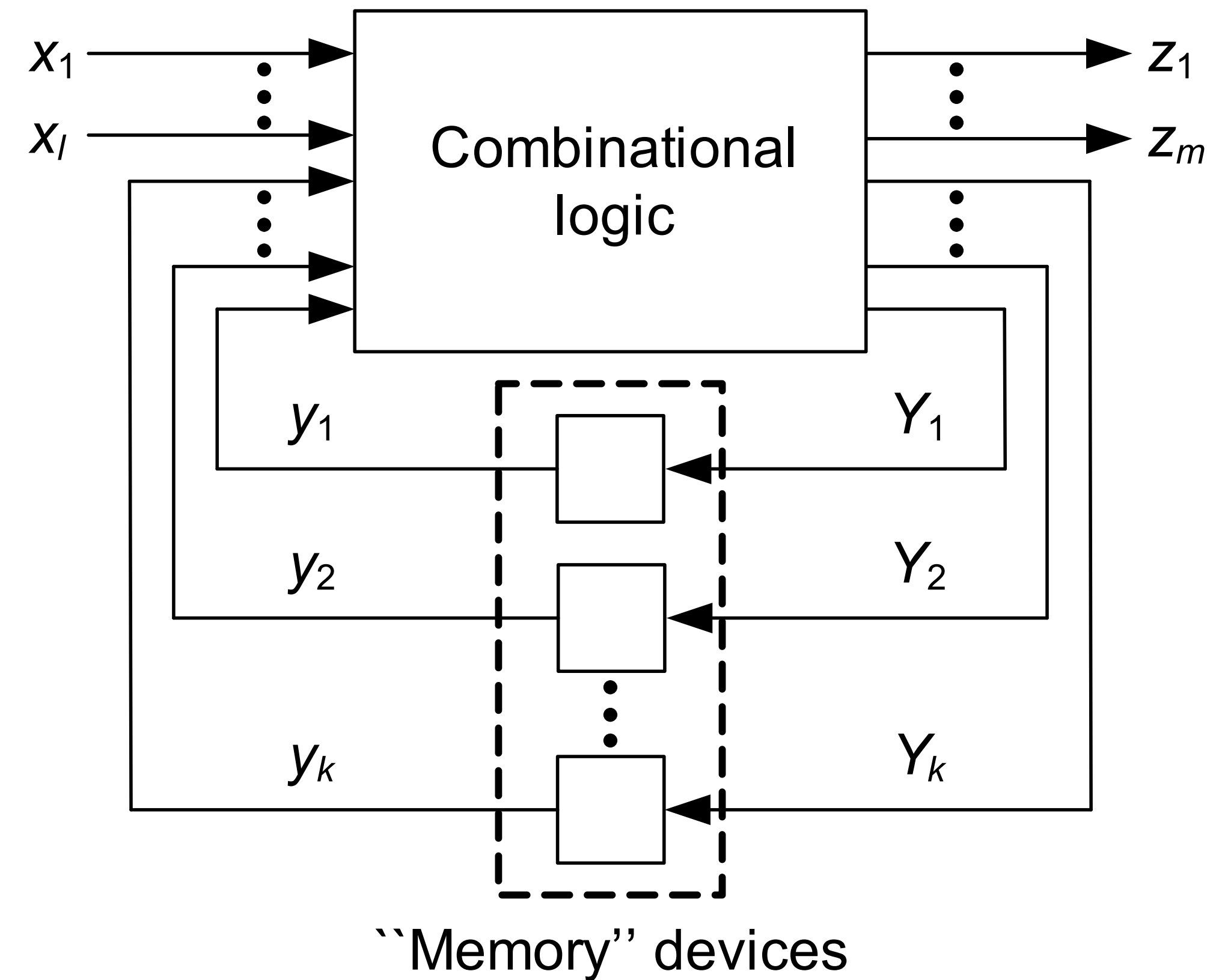
# Sequential Circuits and Finite State Machines




# Memory Element: Latches

**Latch:** remains in one state indefinitely until an input signals directs it to do otherwise


**Set-reset of *SR* latch:**



(a) Block diagram.

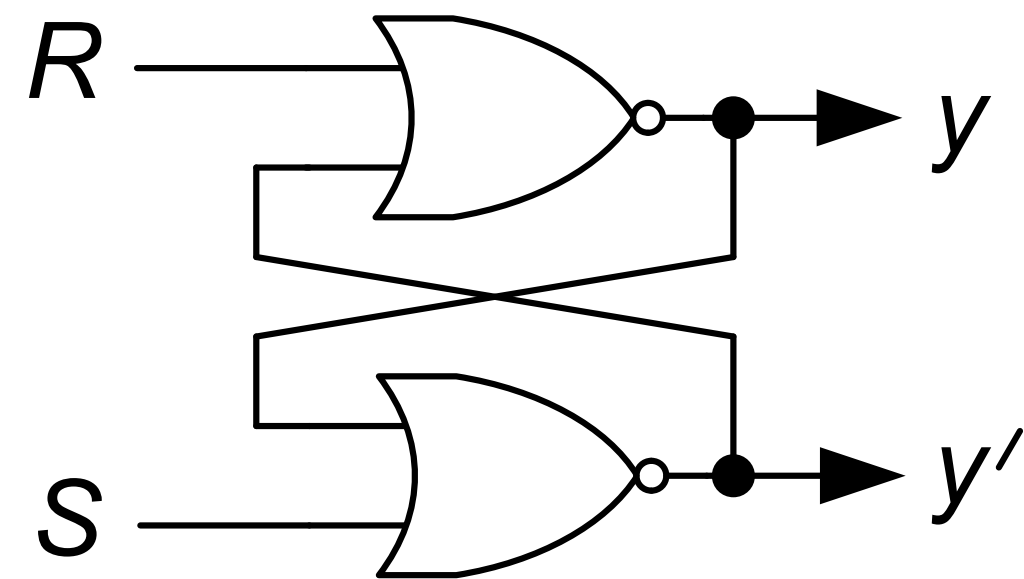

(b) NOR latch.

 

(c) NAND latch.



# Memory Element: Latches

Characteristic table and excitation requirements:

$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1


$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$


<i>Circuit change</i>		<i>Required value</i>	
<i>From:</i>	<i>To:</i>	$S$	$R$
0	0	0	—
0	1	1	0
1	0	0	1
1	1	—	0

**Clocked  $SR$  latch:** all state changes synchronized to clock pulses

 - Restrictions placed on the length and frequency of clock pulses: so that the circuit changes state no more than once for each clock pulse



(a) Block diagram.

 

(b) Logic diagram.



# Memory Element: Latches

Why is the (1,1) input forbidden?


$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1

$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$



# Memory Element: Latches

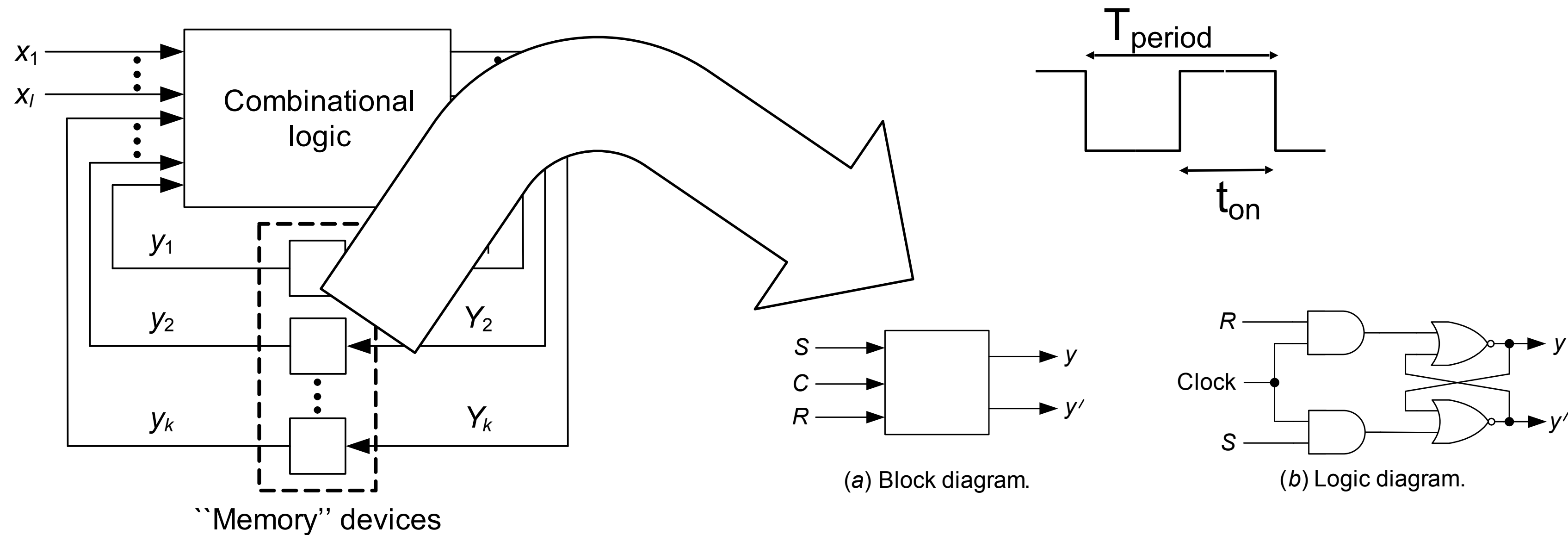


- A **clock** is a periodic signal that is used to keep time in sequential circuits.
- **Duty Cycle** is the ration of  $t_{\text{on}}/T_{\text{period}}$
- We want to keep  $t_{\text{on}}$  small so that in the same clock pulse only a single computation is performed.
- We want to keep  $T_{\text{period}}$  sufficient so that there is enough time for the next input to be computed.


 
# Memory Element: T Latch

Value 1 applied to its input triggers the latch to change state



(a) Block diagram.

(b) Deriving the T latch from the clocked SR latch.

Excitations requirements:

<i>Circuit change</i>		<i>Required value T</i>
<i>From:</i>	<i>To:</i>	
0	0	0
0	1	1
1	0	1
1	1	0

“Q” is basically “y”

Characteristic Table

<b>T Flip-Flop</b>		
<b>T</b>	<b>Q(t + 1)</b>	
0	Q(t)	No change
1	Q'(t)	Complement

$$\begin{aligned}
 y(t+1) &= Ty'(t) + T'y(t) \\
 &= T \oplus y(t)
 \end{aligned}$$




# Memory Element: JK Latch

Unlike the *SR* latch,  $J = K = 1$  is permitted: when it occurs, the latch acts like a trigger and switches to the complement state



(a) Block diagram.

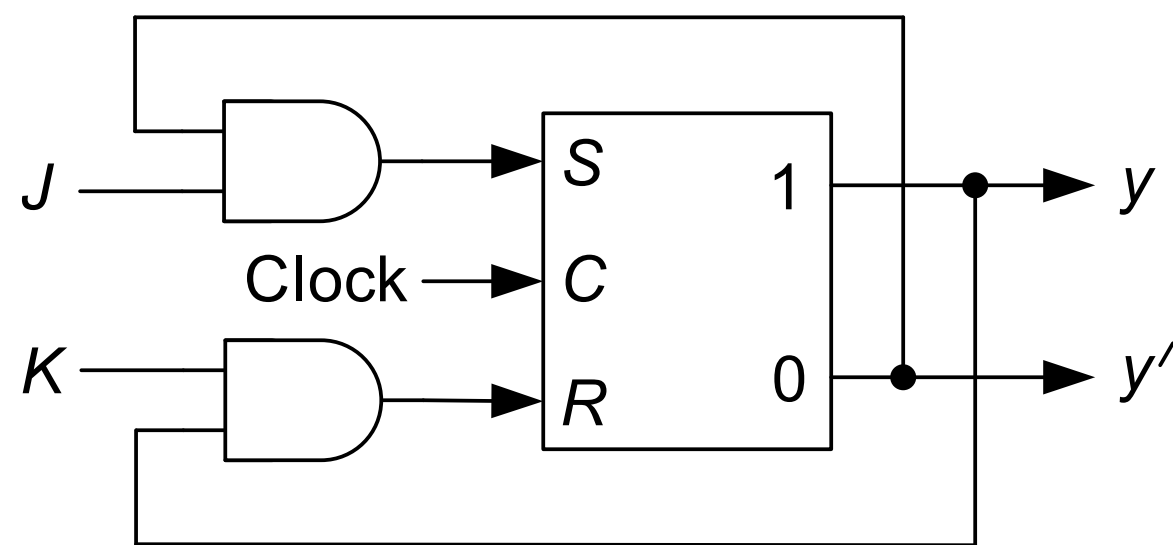

(b) Constructing the JK latch from the clocked SR latch.

## Excitation requirements:

Circuit change		Required value	
From:	To:	<i>J</i>	<i>K</i>
0	0	0	–
0	1	1	–
1	0	–	1
1	1	–	0

“Q” is basically “y”

## Characteristic Table


<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	<i>Q</i> ( <i>t</i> + 1)	
0	0	<i>Q</i> ( <i>t</i> )	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q</i> '( <i>t</i> )	Complement

Can you write the characteristic equation?



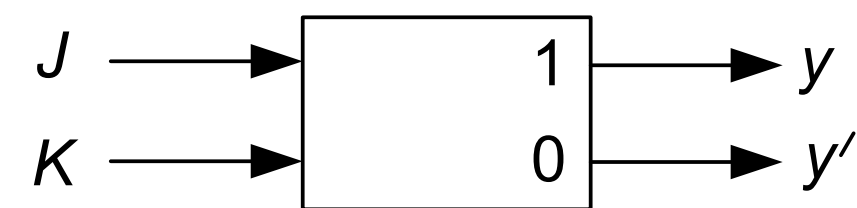
# Memory Element: JK Latch

Unlike the *SR* latch,  $J = K = 1$  is permitted: when it occurs, the latch acts like a trigger and switches to the complement state



(a) Block diagram.

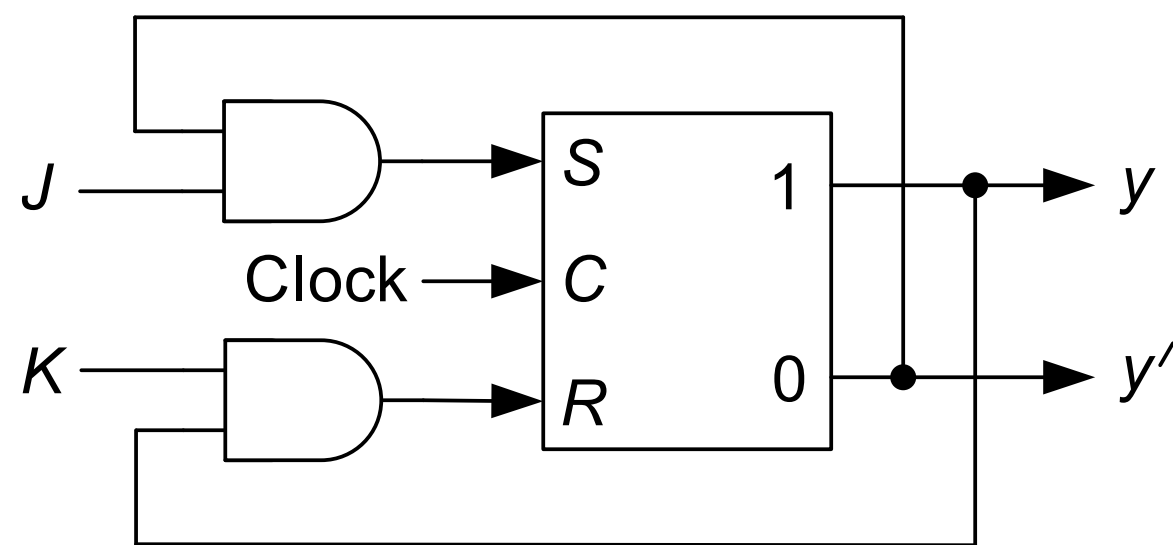

(b) Constructing the JK latch from the clocked SR latch.

## Excitation requirements:

Circuit change		Required value	
From:	To:	J	K
0	0	0	–
0	1	1	–
1	0	–	1
1	1	–	0

“Q” is basically “y”

Can you write the characteristic equation?

## Characteristic Table

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement


$$y(t + 1) = Jy(t)' + K'y(t)$$




# D Latch — The Latch of Your Life

The next state of the  $D$  latch is equal to its present excitation:  
 $y(t+1) = D(t)$

<b><math>D</math> Flip-Flop</b>		
<b><math>D</math></b>	<b><math>Q(t + 1)</math></b>	
0	0	Reset
1	1	Set

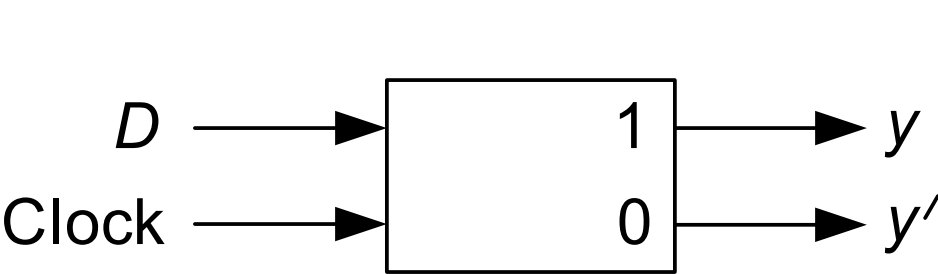

(a) Block diagram.

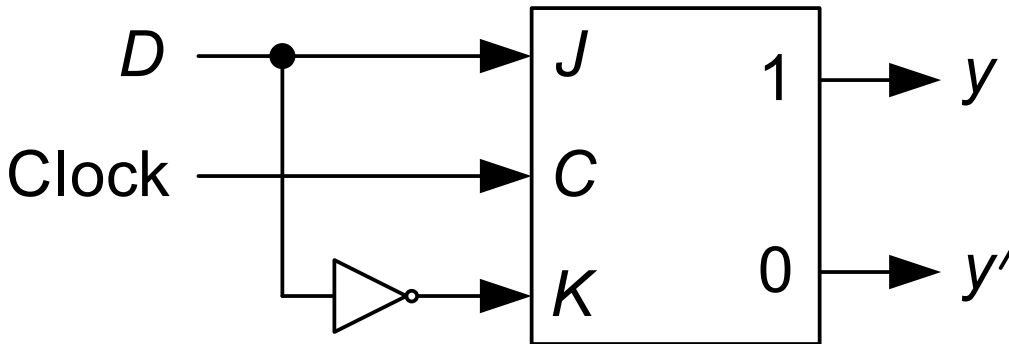

(b) Transforming the JK latch to the D latch.

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1



# How is Your Clock?


**Clocked latch:** changes state only in synchronization with the clock pulse and no more than once during each occurrence of the clock pulse

**Duration of clock pulse:** determined by circuit delays and signal propagation time through the latches

- Must be long enough to allow latch to change state, and
- Short enough so that the latch will not change state twice due to the same excitation

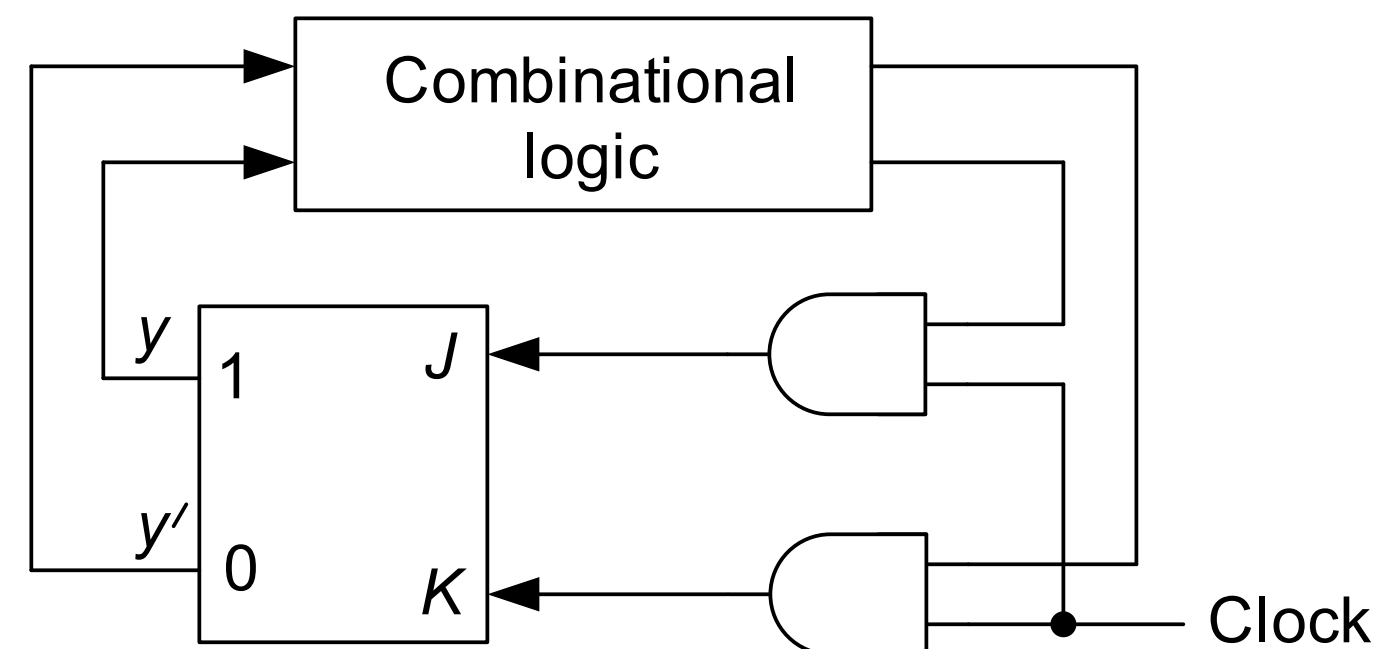**Excitation of a *JK* latch within a sequential circuit:**


- Length of the clock pulse must allow the latch to generate the  $y$ 's
- But should not be present when the values of the  $y$ 's have propagated through the combinational circuit




# Master Slave Flip-Flop

**Master-slave flip-flop:** a type of synchronous memory element that eliminates the timing problems by isolating its inputs from its outputs

**Master-slave *SR* flip-flop:**

 

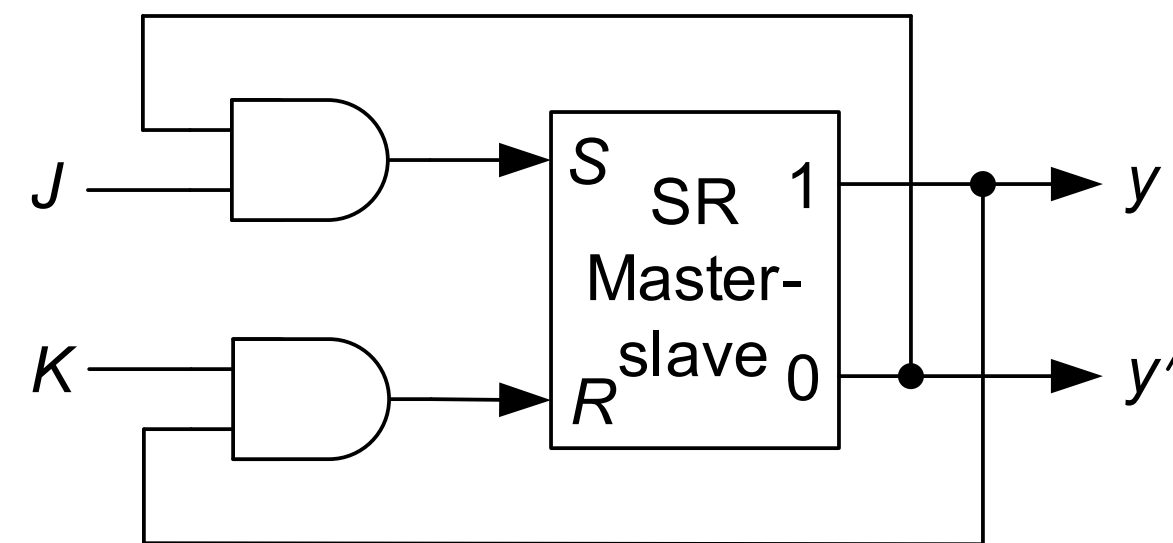**Master-slave *JK* flip-flop:** since master-slave *SR* flip-flop suffers from the problem that both its inputs cannot be 1, it can be converted to a *JK* flip-flop






# Edge Triggered Flip-Flop

**Positive (negative) edge-triggered  $D$  flip-flop:** stores the value at the  $D$  input when the clock makes a 0  $\rightarrow$  1 (1  $\rightarrow$  0) transition


- Any change at the  $D$  input after the clock has made a transition does not have any effect on the value stored in the flip-flop

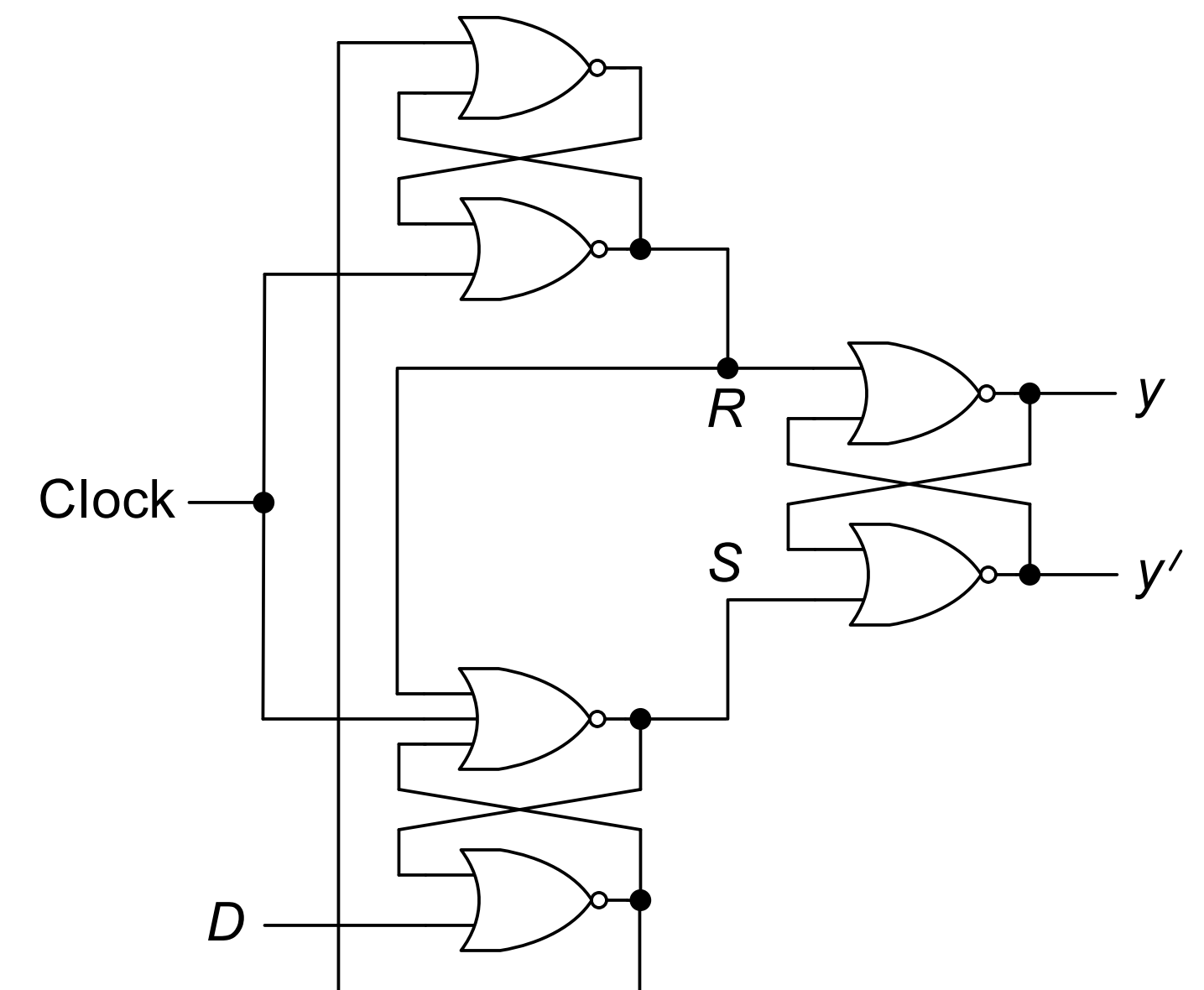**A negative edge-triggered  $D$  flip-flop:**

- When the clock is high, the output of the bottommost (topmost) NOR gate is at  $D'$  ( $D$ ), whereas the  $S$ - $R$  inputs of the output latch are at 0, causing it to hold previous value
- When the clock goes low, the value from the bottommost (topmost) NOR gate gets transferred as  $D$  ( $D'$ ) to the  $S$  ( $R$ ) input of the output latch
  - Thus, output latch stores the value of  $D$
- If there is a change in the value of the  $D$  input after the clock has made its transition, the bottommost NOR gate attains value 0
  - However, this cannot change the  $SR$  inputs of the output latch




# Edge Triggered Flip-Flop

 

Changes to the input  $D$  does not affect the output  $y$  and  $y'$  when the clock is high.



# Edge Triggered Flip-Flop

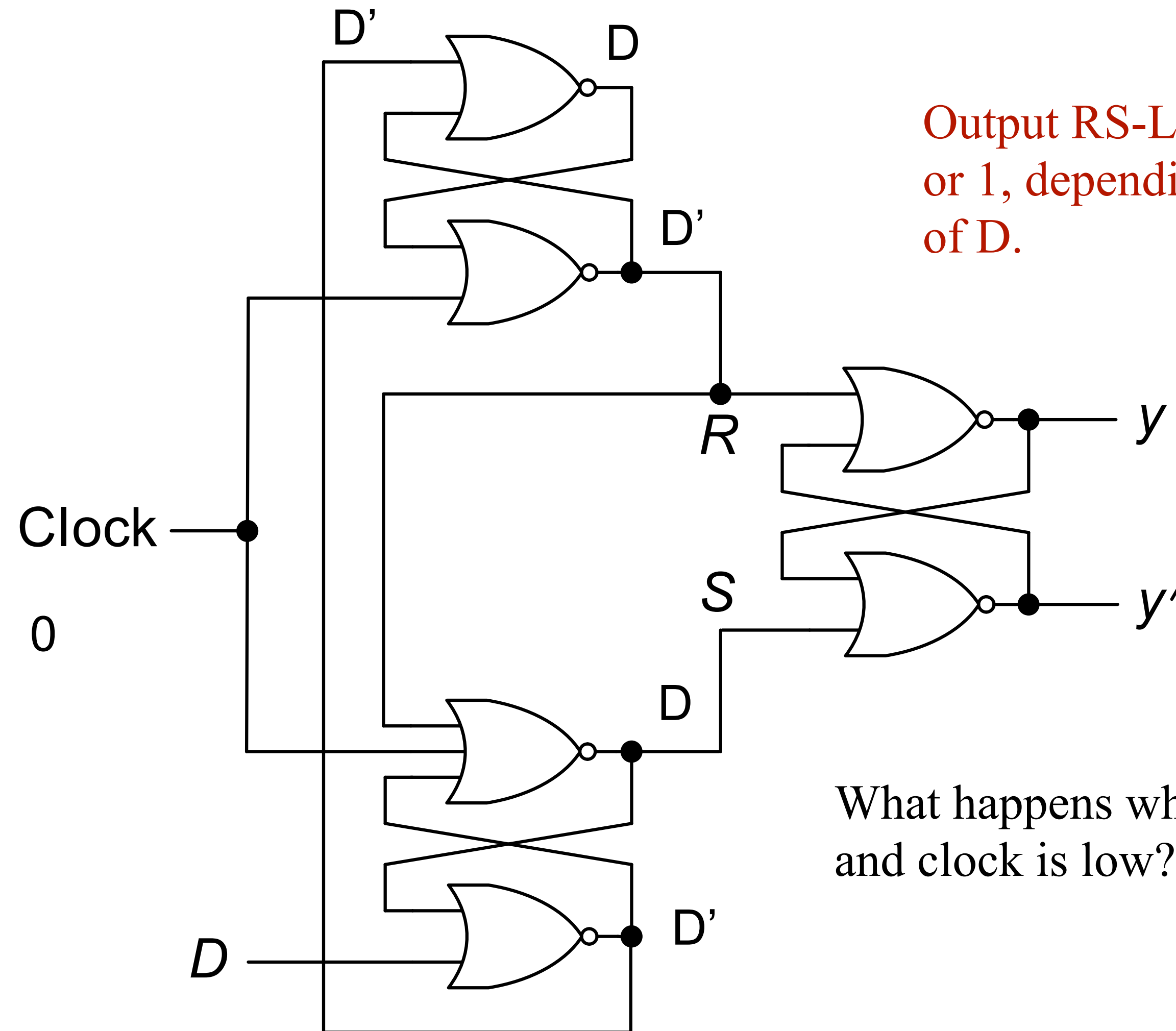

Output RS-Latch stores a 0 or 1, depending on the value of D.

What happens when D changes and clock is low?