Digital Logic Design + Computer Architecture

Sayandeep Saha

Assistant Professor
Department of Computer Science and Engineering
Indian Institute of Technology Bombay

Logic Minimization

Life of an Engineer

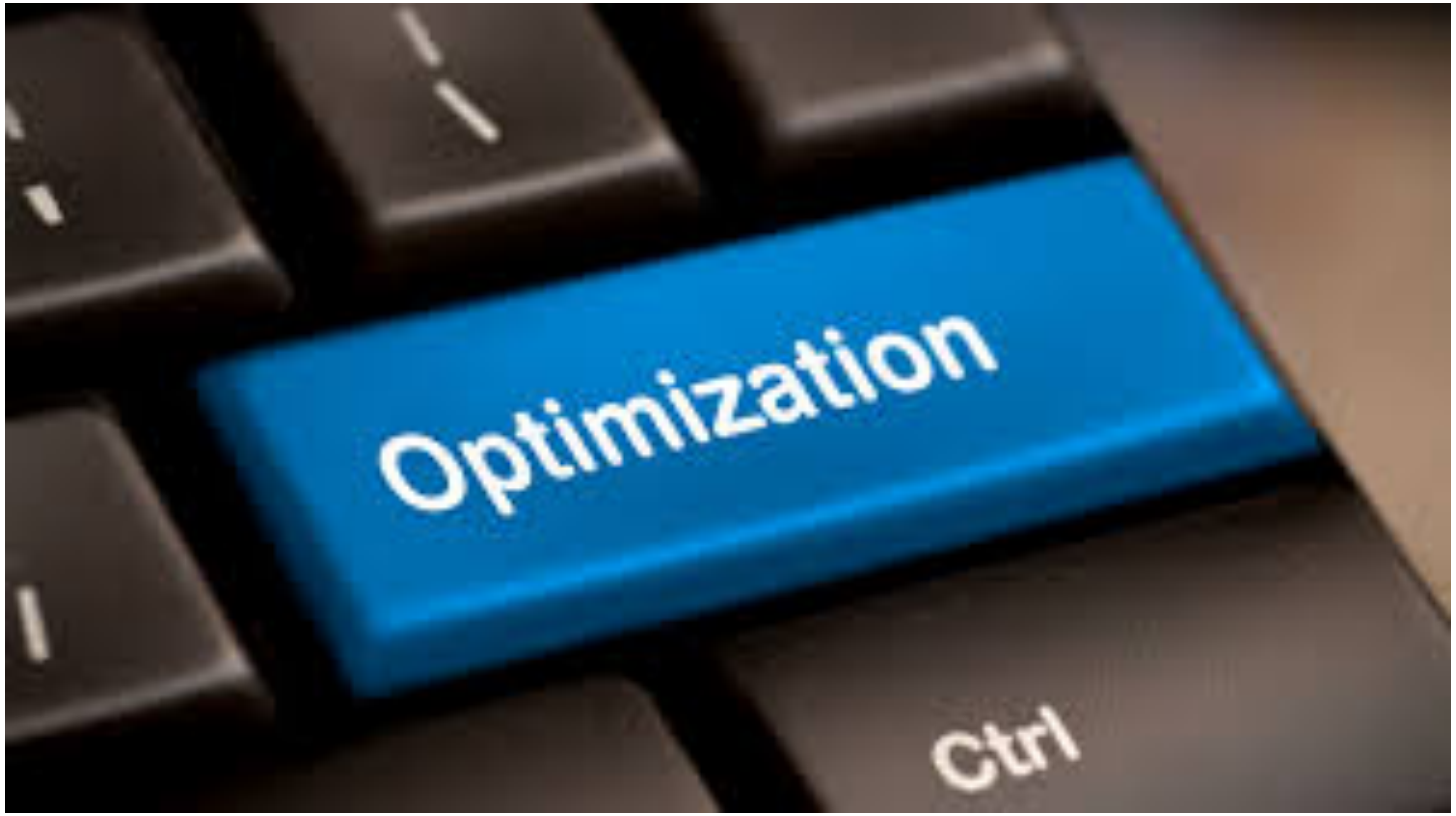

Logic Minimization: Why?

- Consider a switching expression. **How many gates do you need to implement this?** Consider each gate is 2-input, 1 output except the NOTs — 5 OR, 12 ANDs, 3 NOTs

$$f(x, y, z) = x'yz' + x'y'z' + xy'z' + x'yz + xyz + xy'z$$

- Now consider the following expression:’ $x'z' + y'z' + yz + xz$
- Observe that both implements the same logic function!!! Now you need 4 ORs, 4 ANDs, and 3 NOTs.
- Can you do better?? — Yes $f(x, y, z) = x'z' + xy' + yz$
- Turns out that there can be more such expressions.
- Lower gate count => Lower transistor count => Lower area (and perhaps less power, and time)…
- So, now we have an engineering problem in hand — **how to minimize the switching expressions???**

Bigger Picture

- Modern circuits contains billions of gates — e.g. AMD Instinct is a GPU processor containing 146,000,000,000 transistors; so a few billions of gates (if not trillions)…
- How do people minimized their gate network…Fortunately we have tools for that.
- Today we will be studying some of the fundamental techniques behind these tools.
    - Of course, a very very rudimentary intro

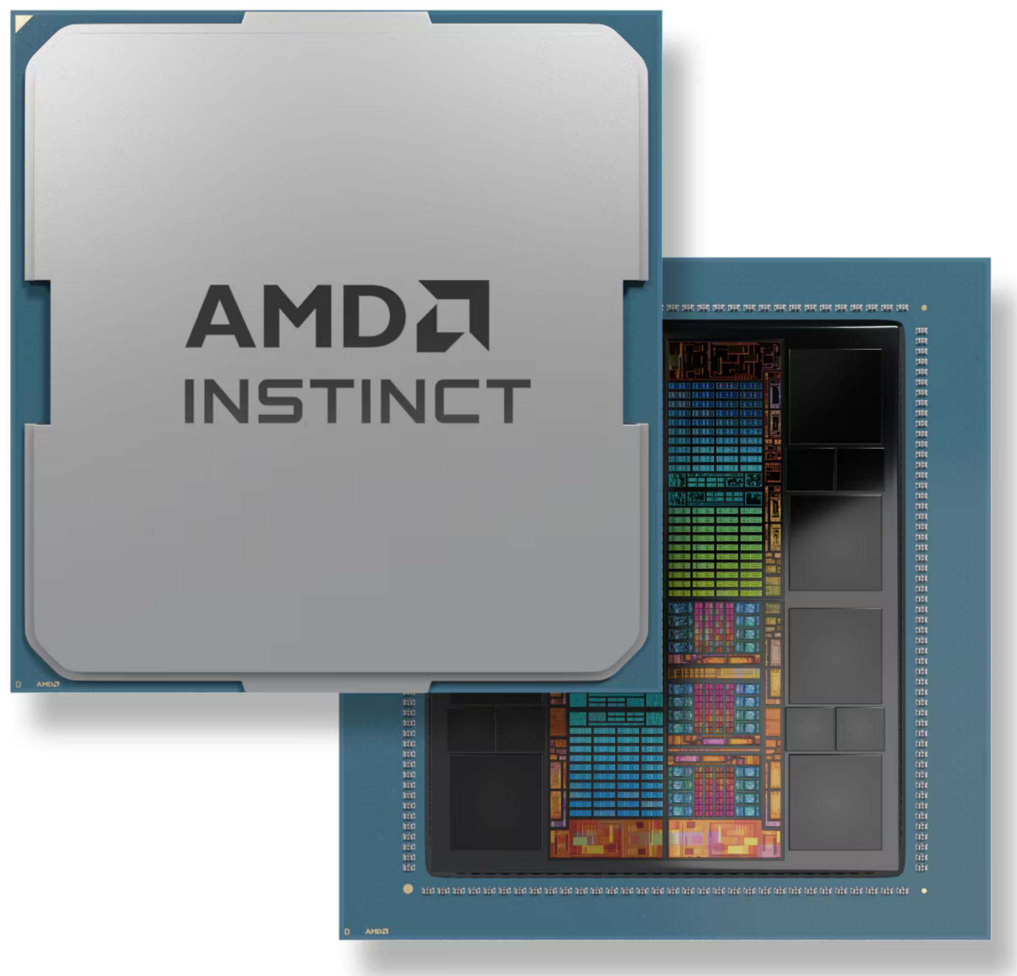

Bigger Picture

- Modern circuits contains billions of gates — e.g. AMD Instinct is a GPU processor containing 146,000,000,000 transistors; so a few billions of gates (if not trillions)…
- How do people minimized their gate network…Fortunately we have tools for that.
- Today we will be studying some of the fundamental techniques behind these tools.

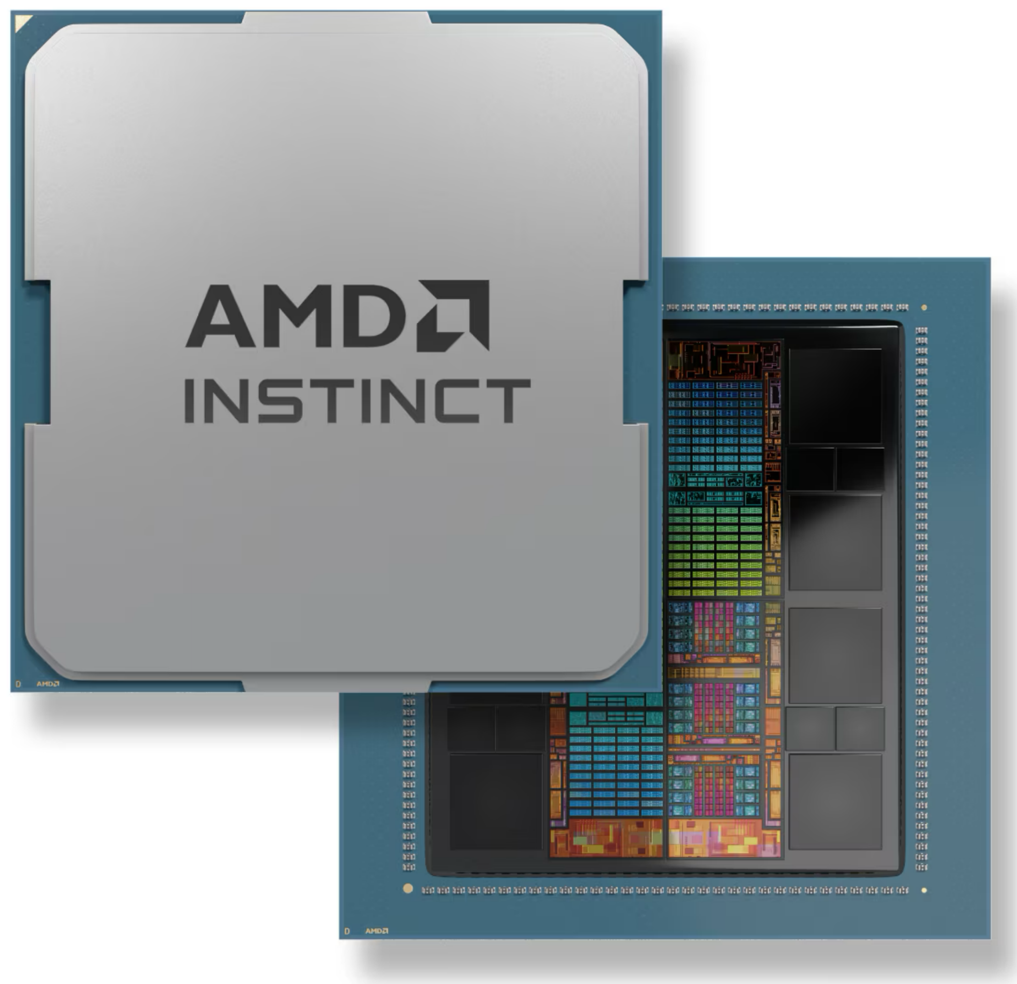

Bigger Picture

- Modern circuits contains billions of gates — e.g. AMD Instinct is a GPU processor containing 146,000,000,000 transistors; so a few billions of gates (if not trillions)…
- How do people minimized their gate network…Fortunately we have tools for that.
- Today we will be studying some of the fundamental techniques behind these tools.

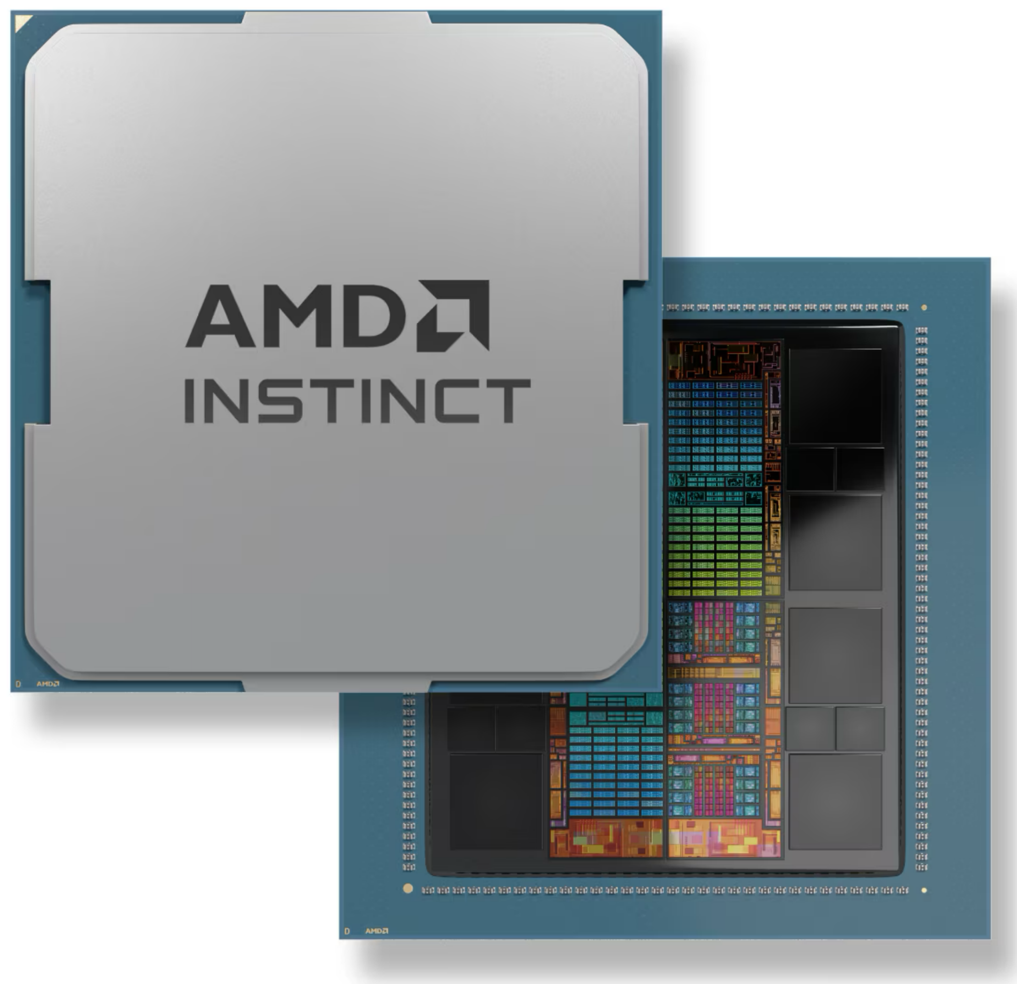

The Map Method

- **Karnaugh map**: modified form of truth table
- Combine terms using the **Aa + Aa’ = A (combining theorem)**

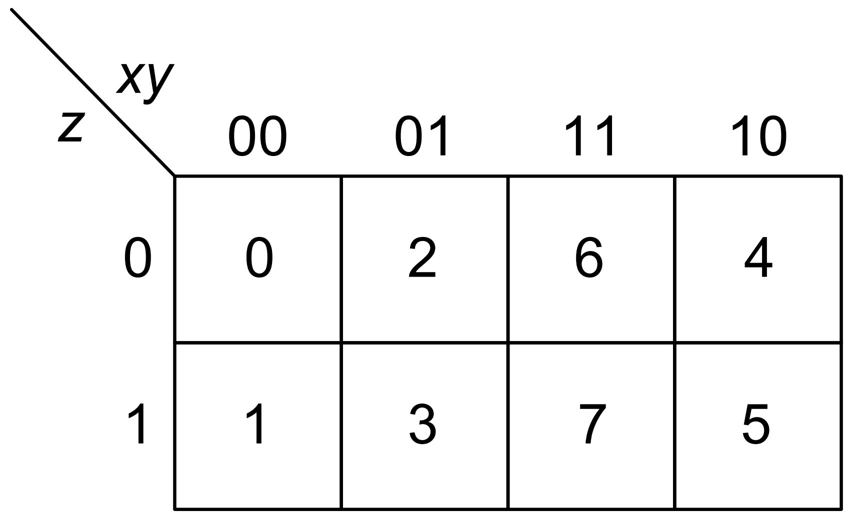

(a) Location of minterms in a three-variable map.

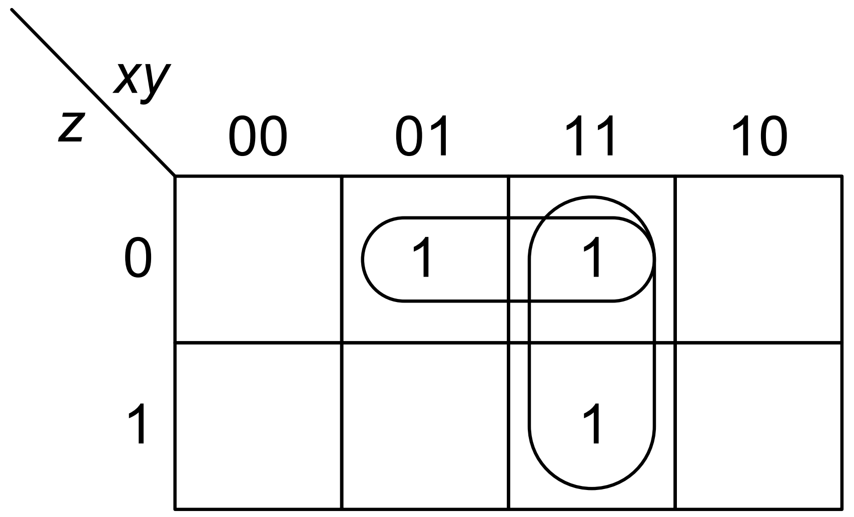

(b) Map for function $f(x,y,z) = \sum(2,6,7) = yz' + xy$.

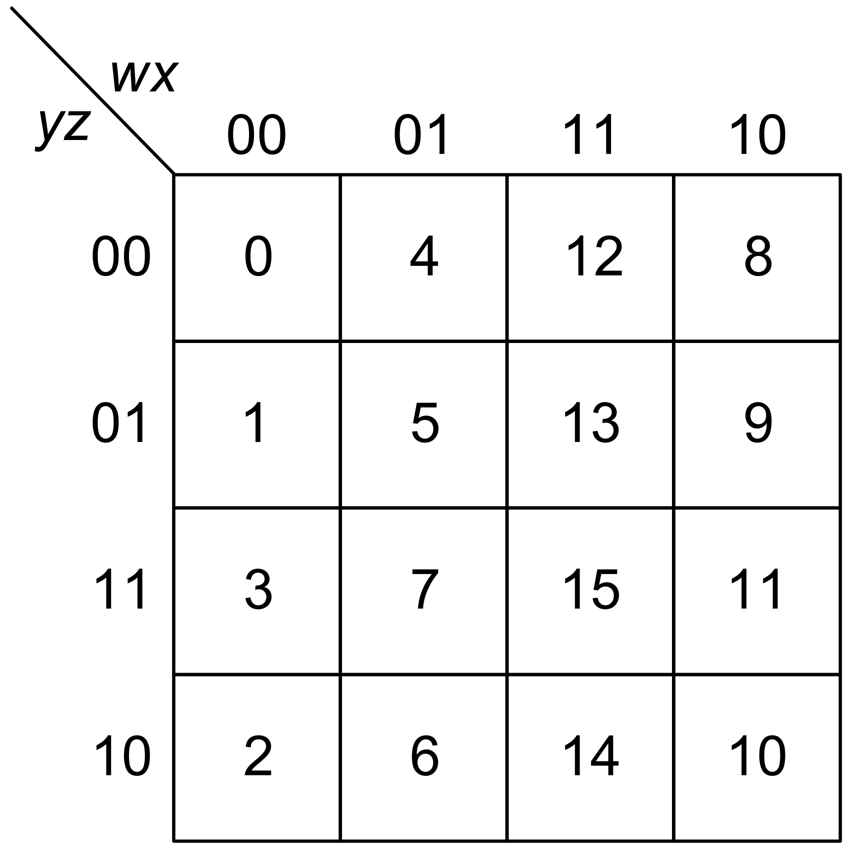

(c) Location of minterms in a four-variable map.

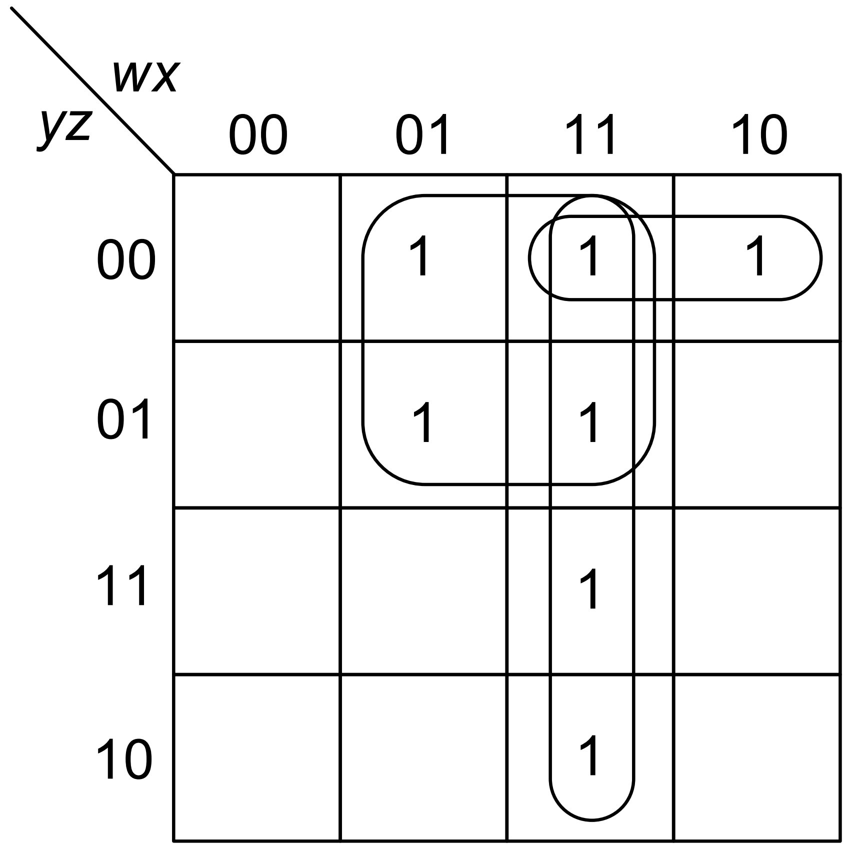

(d) Map for function $f(w,x,y,z) = \sum(4,5,8,12,13,14,15) = wx + xy' + wy'z'$.

The Map Method

- **Karnaugh map**: modified form of truth table
- Combine terms using the **Aa + Aa’ = A (combining theorem)**
- **<u>Cube</u>**:
  - Collection of **2^m** cells, each adjacent to ***m*** cells of the collection
  - The cube is said to **cover** the cells it is involved with
  - Expressed by a product of **n-m literals** for a function containing **n variables**
  - **m literals** not in the product said to be eliminated

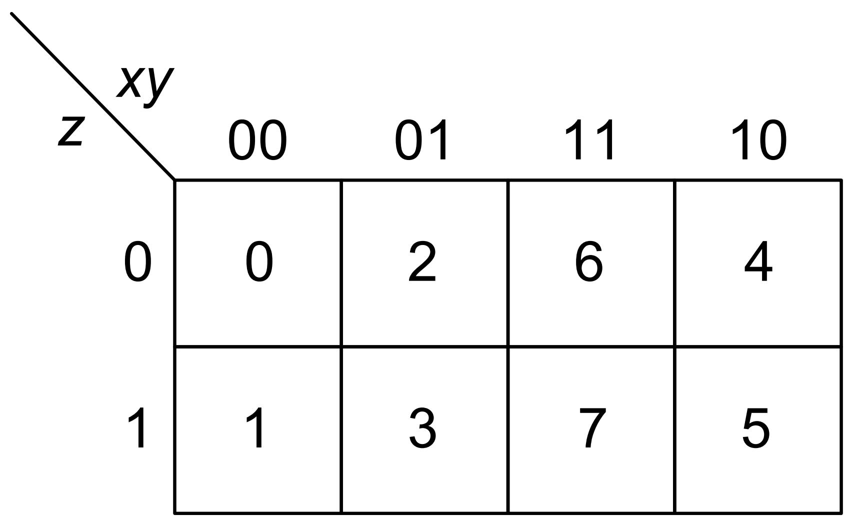

(*a*) Location of minterms in a three-variable map.

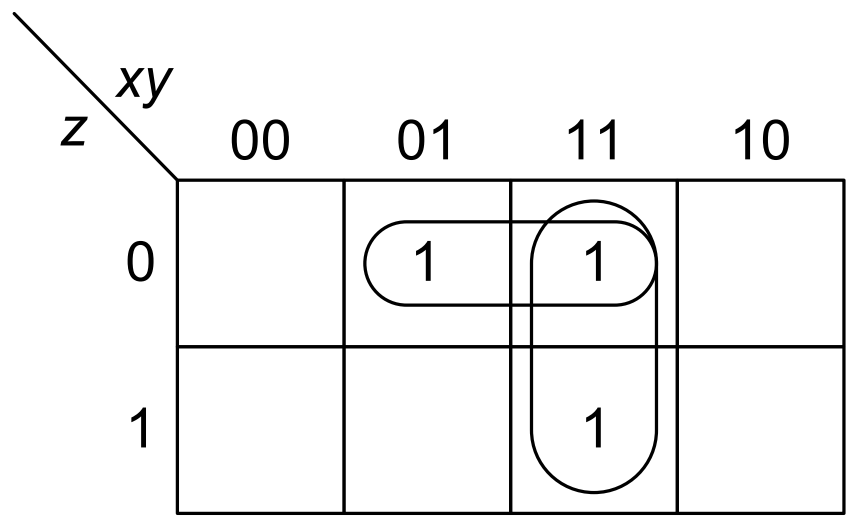

(*b*) Map for function $f(x,y,z) = \sum(2,6,7) = yz' + xy$.

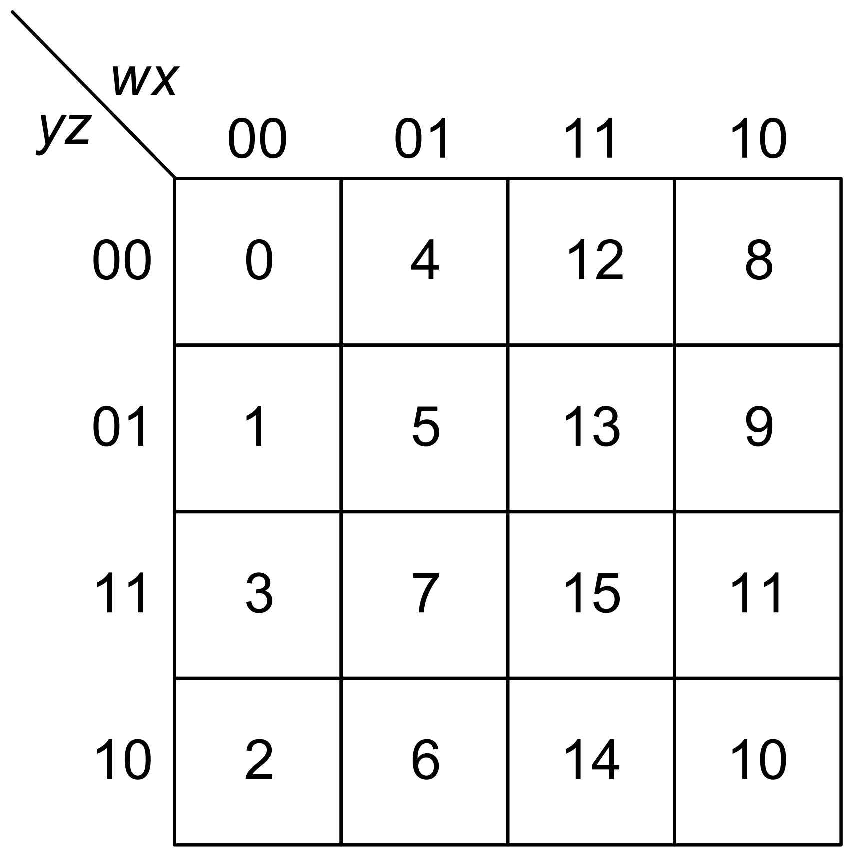

(*c*) Location of minterms in a four-variable map.

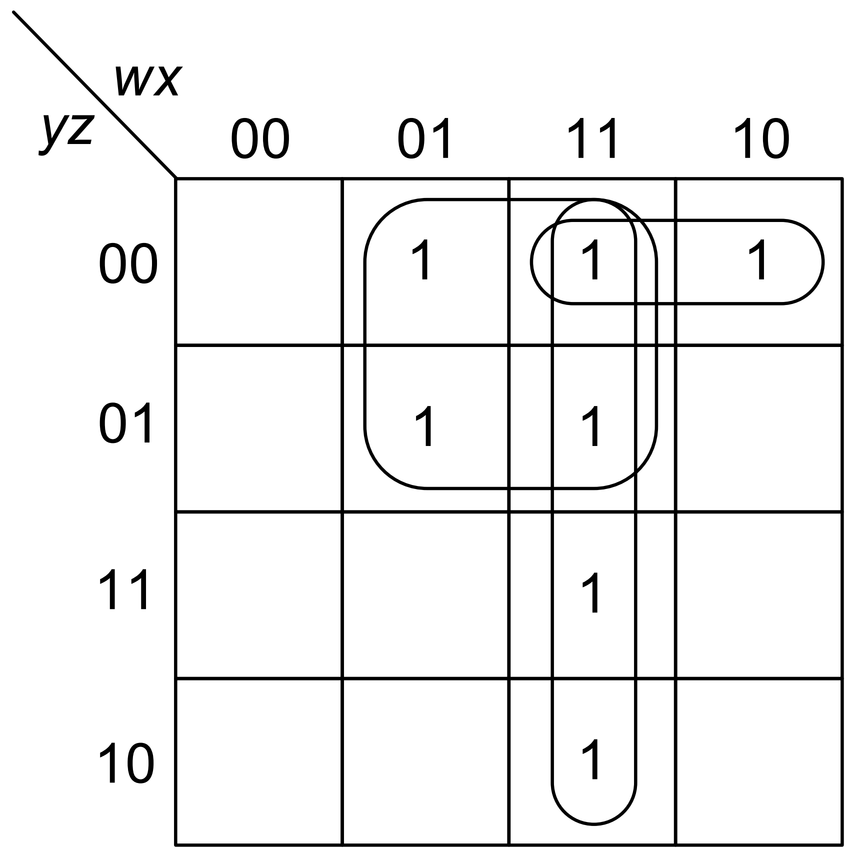

(*d*) Map for function $f(w,x,y,z) = \sum(4,5,8,12,13,14,15) = wx + xy' + wy'z'$.

The Map Method

- **Karnaugh map**: modified form of truth table
- Combine terms using the **Aa + Aa’ = A (combining theorem)**
- **<u>Cube</u>**:
  - Collection of $\mathbf{2}^{\boldsymbol{m}}$ cells, each adjacent to ***m*** cells of the collection
  - The cube is said to **cover** the cells it is involved with
  - Expressed by a product of **n-m literals** for a function containing **n variables**
  - **m literals** not in the product said to be eliminated
  - **More Clarification**:
    - Consider the squares 2 and 6 in Fig (a)
    - The minterms are z’x’y and z’xy
    - Now apply the **combining theorem.**
    - Literal x and x’ are eliminated.
    - The result is a 2-cube.

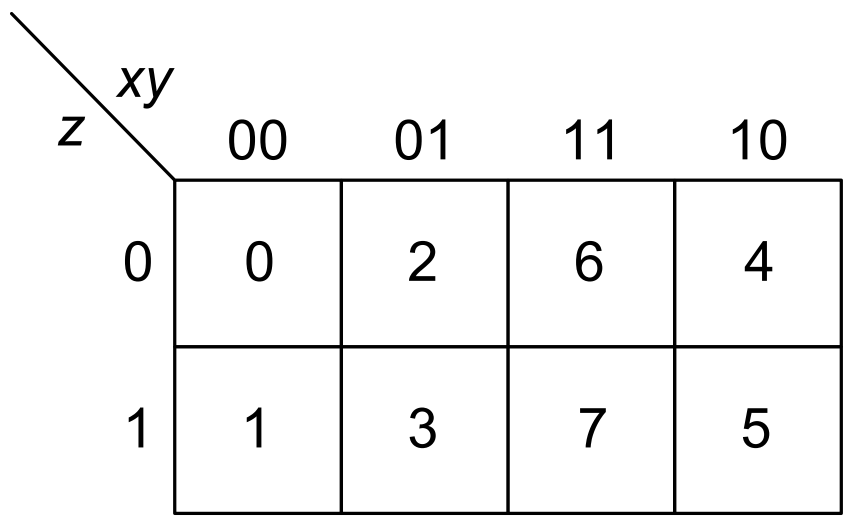

(a) Location of minterms in a three-variable map.

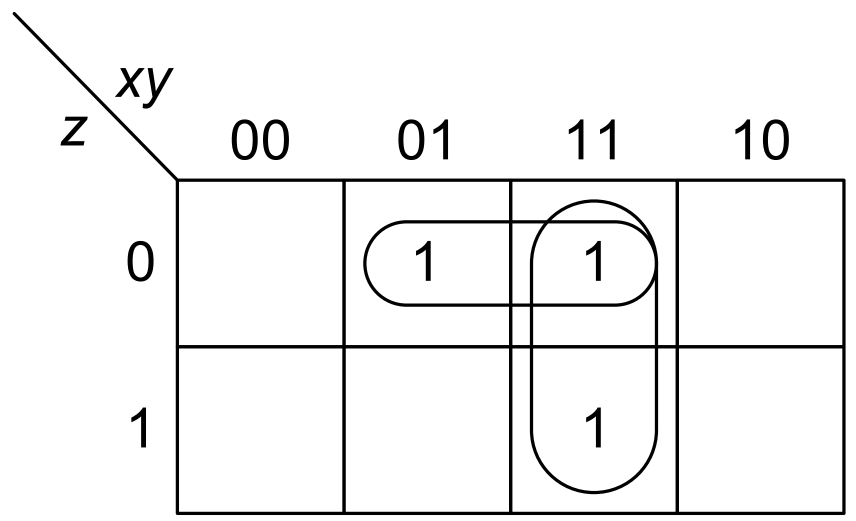

(b) Map for function $f(x,y,z) = \sum(2,6,7) = yz' + xy$.

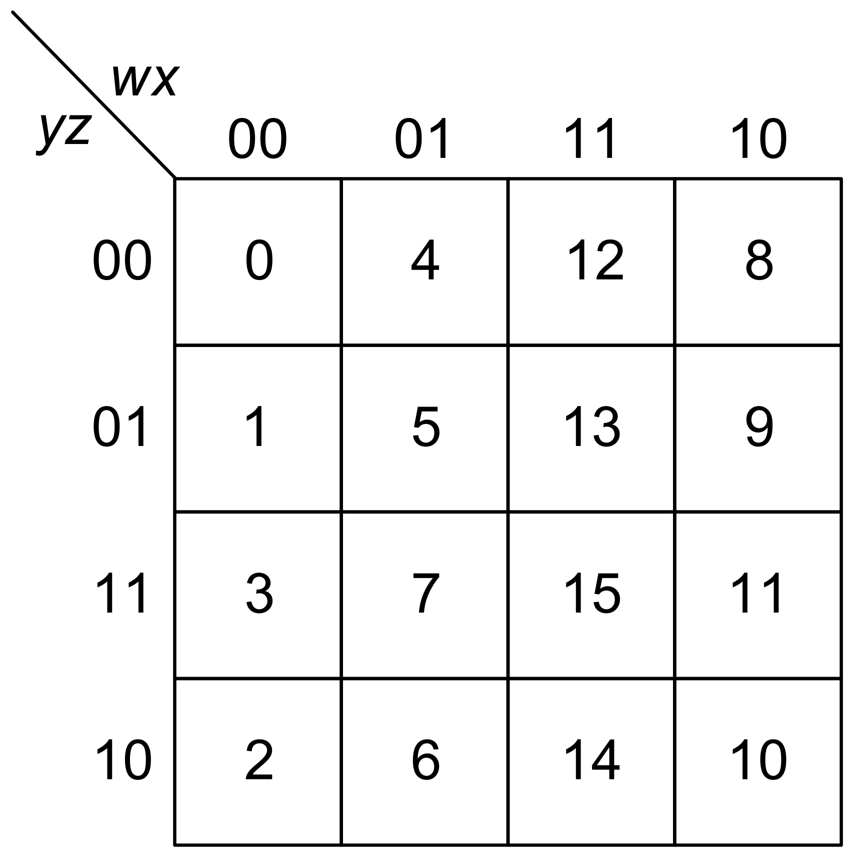

(c) Location of minterms in a four-variable map.

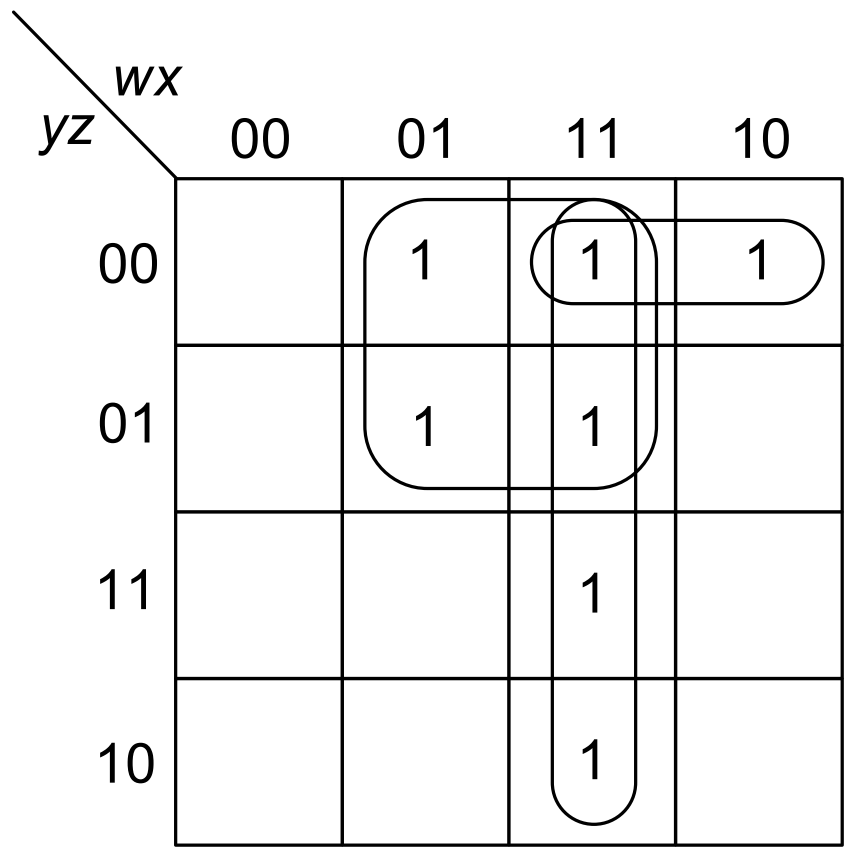

(d) Map for function $f(w,x,y,z) = \sum(4,5,8,12,13,14,15) = wx + xy' + wy'z'$.

The Map Method

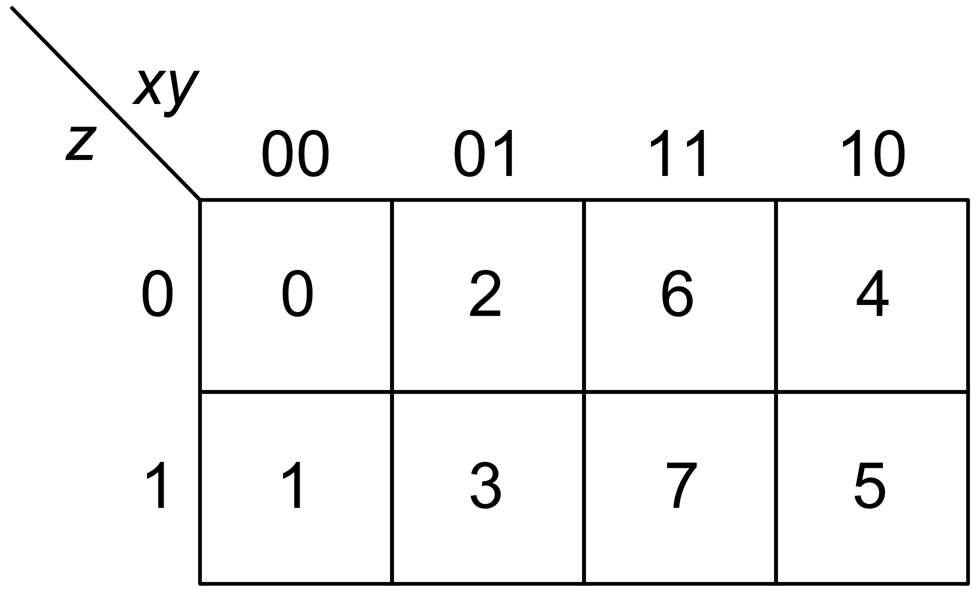

(a) Location of minterms in a three-variable map.

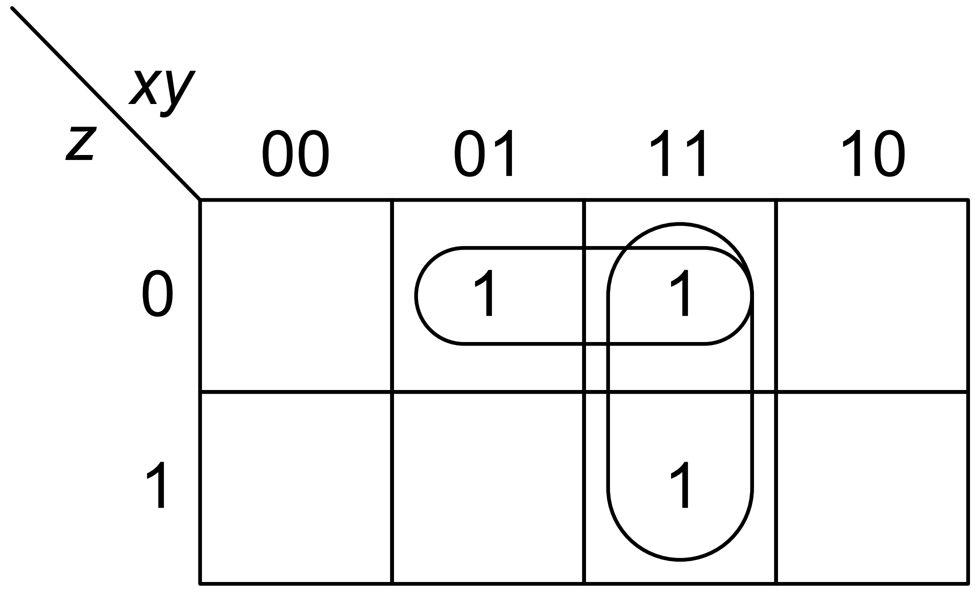

(b) Map for function $f(x,y,z) = \sum(2,6,7) = yz' + xy$.

- **Example**: $f = yz' + xy$
  - **Use of cell 6 in forming both cubes justified by idempotent law**
  - Corresponding algebraic manipulations:

$$
\begin{aligned}
f &= x'yz' + xyz' + xyz \\
&= x'yz' + \underline{xyz' + xyz'} + xyz \text{ (idempotent law)} \\
&= yz'(x' + x) + xy(z' + z) \\
&= yz' + xy
\end{aligned}
$$

The Map Method

- **Example**: w’xy’z’ + w’xy’z + wxy’z’ + wxy’z = xy’(w’z’ + w’z + wz’ + wz) = xy’
- **Trick**:
    - In a cube, just keep the variables not changing their value.

yz \ wx	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

(c) Location of minterms in a four-variable map.

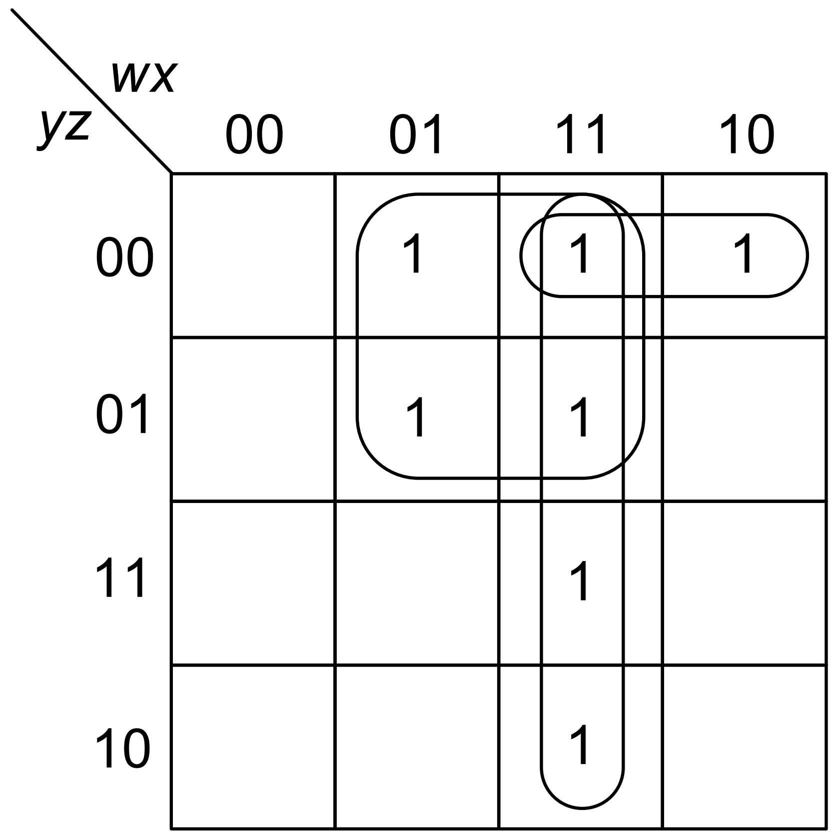

(d) Map for function $f(w,x,y,z) = \sum(4,5,8,12,13,14,15) = wx + xy' + wy'z'$.

The Map Method

Rules for minimization:

- **Step 1**: cover those 1 cells by cubes that cannot be combined with other 1 cells; continue to 1 cells that have a single adjacent 1 cell (thus can form cubes of only two cells)
- **Step 2—:** Combine 1 cells that yield cubes of four cells, but are not part of any cube of eight cells, and so on..
  - A cube contained in a larger cube must never be selected
  - A cube contained in any combination of other cubes already selected in the cover is redundant (**consensus theorem)**
  - If there are more than one way of covering the map with cubes, select the cover with larger cubes
  - **Minimal expression**: collection of cubes that are as large and as few in number as possible, such that each 1 cell is covered by at least one cube
  - **Irredundant expressions**:
    - An SOP from where no term or literal can be deleted.
    - Not necessarily minimal
  - **Minimal and irredundant expressions may not be unique**
  - **But a minimal expression is always irredundant.**

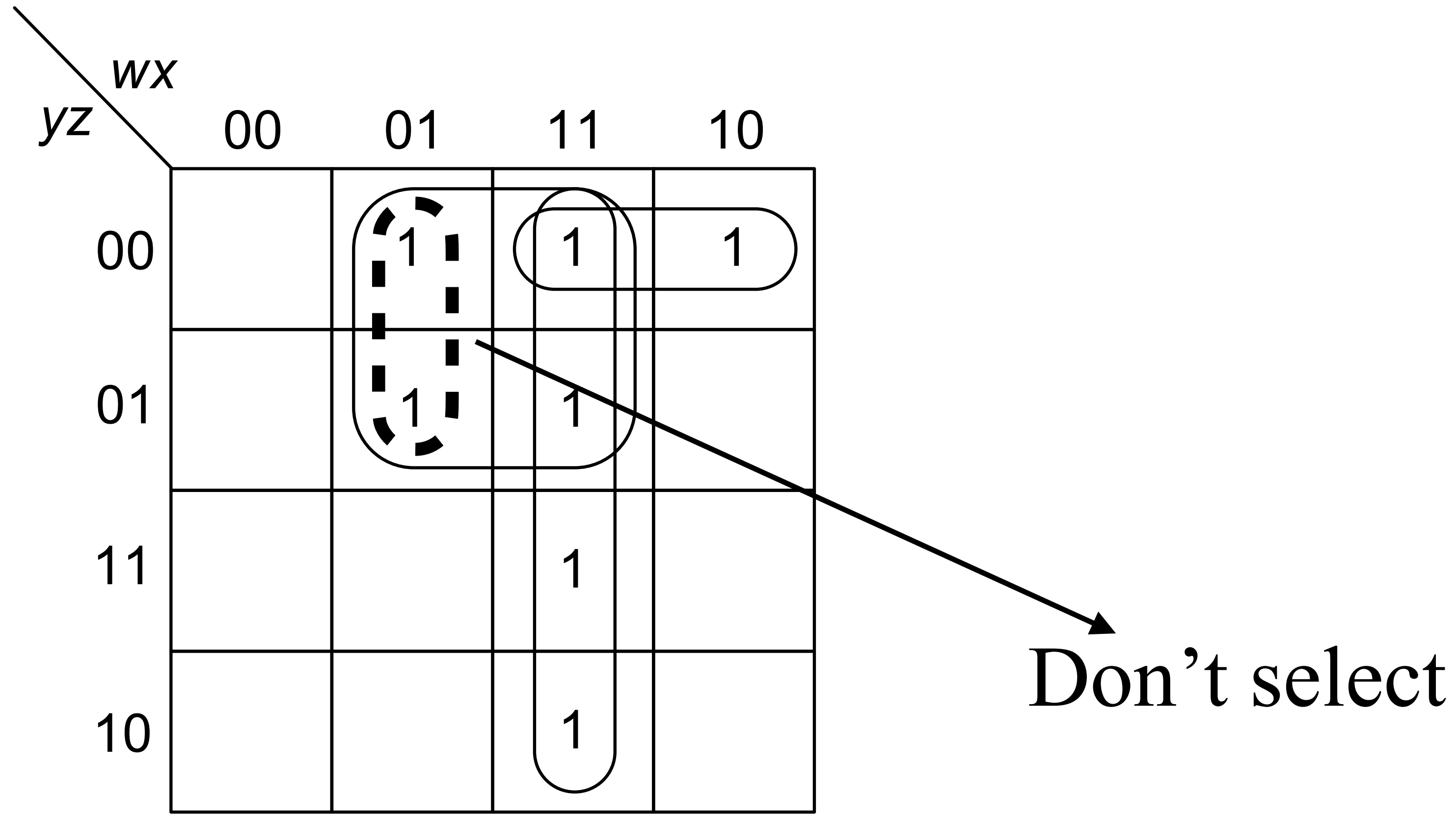

(d) Map for function $f(w,x,y,z)$ $=\sum(4,5,8,12,13,14,15) = wx + xy' + wy'z'$.

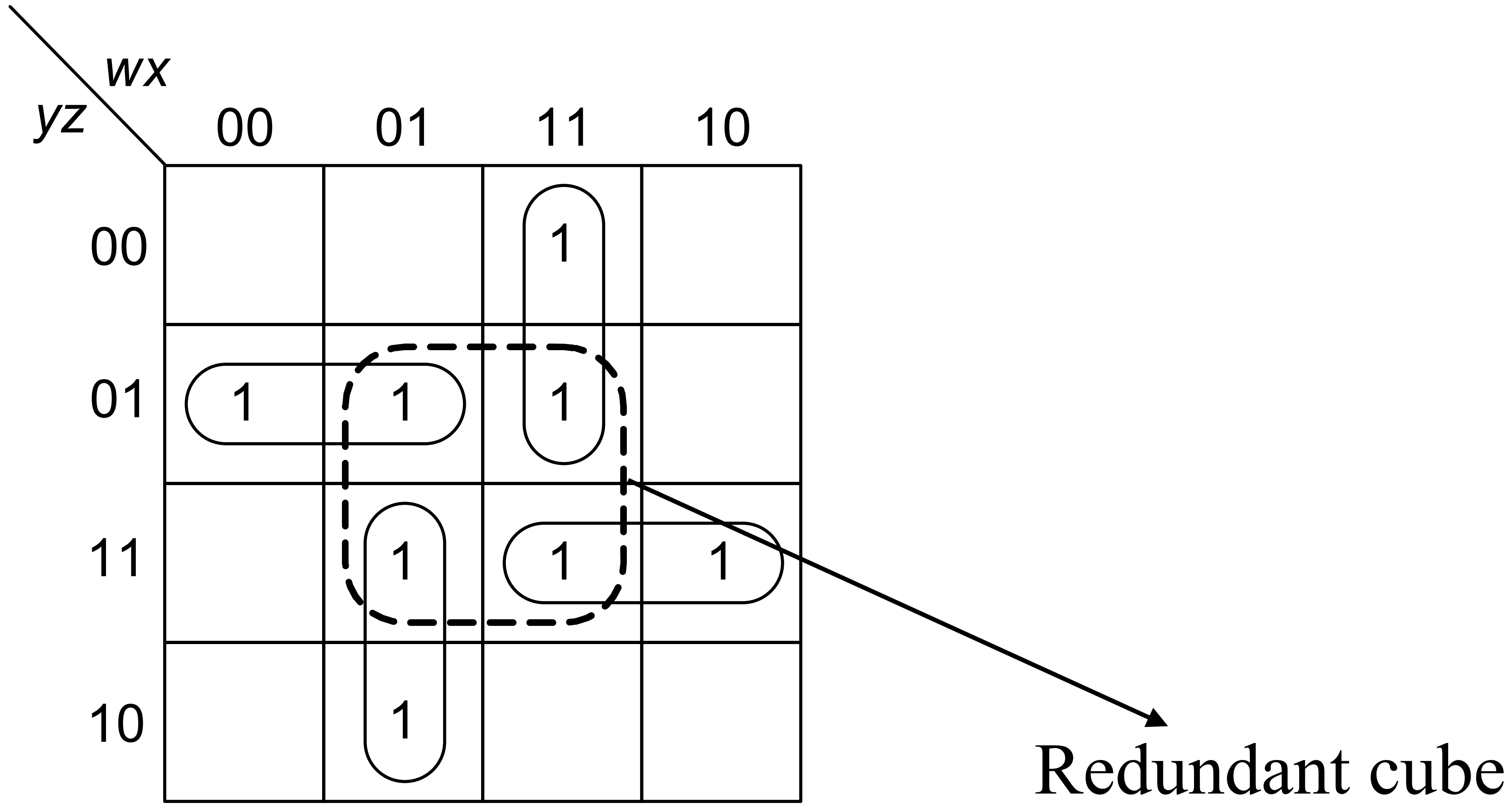

Let's try this..

The Map Method

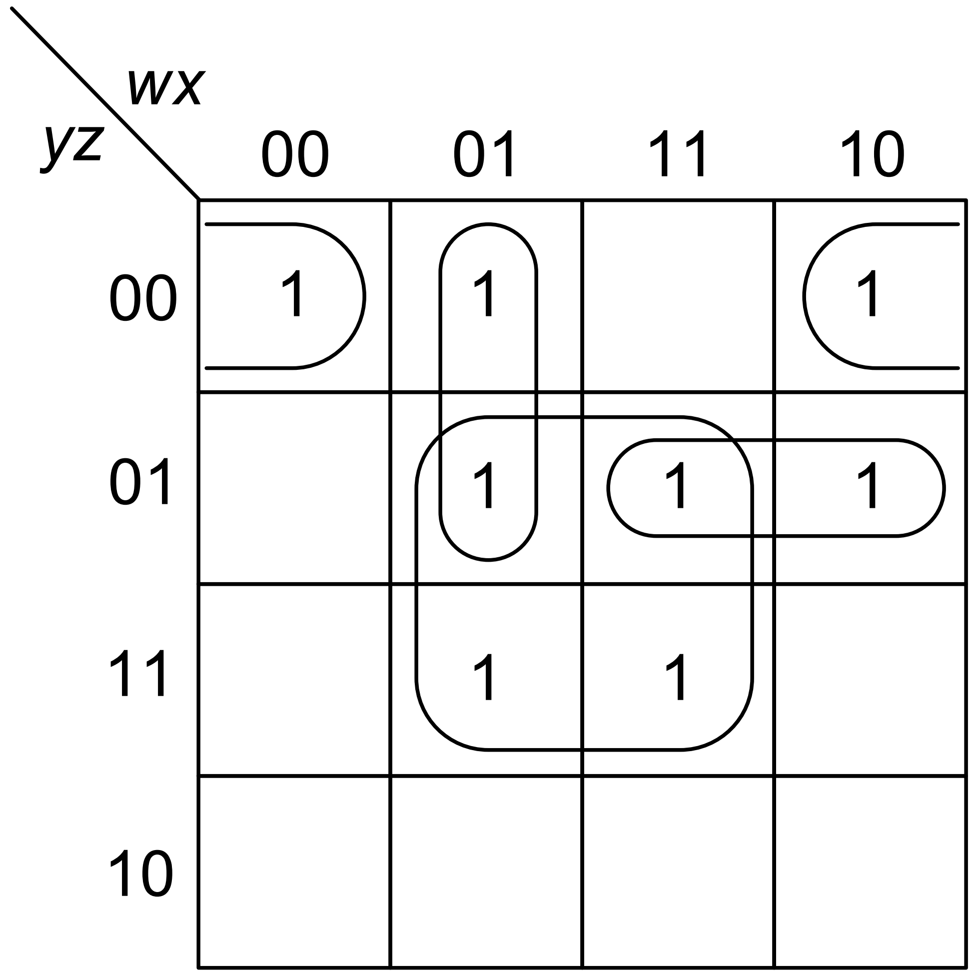

(a) $f = x'y'z' + w'xy' + wy'z + xz$
is an irredundant expression.

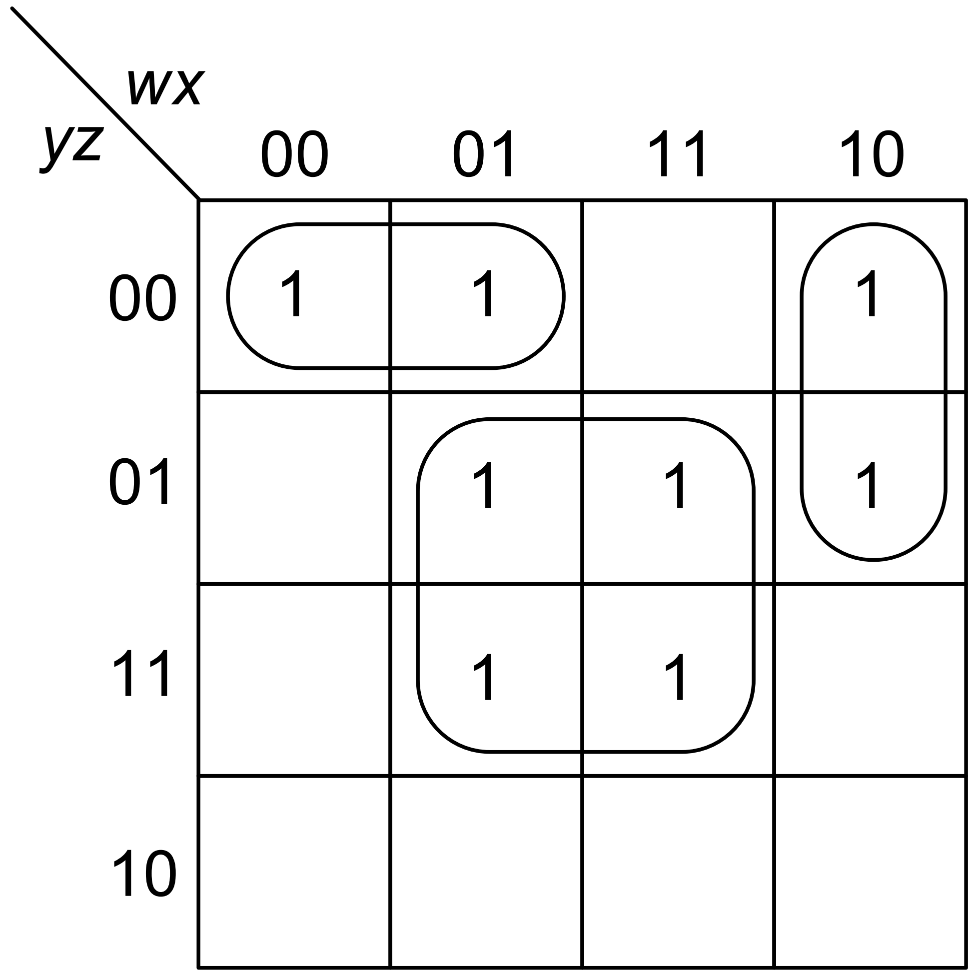

(b) $f = w'y'z' + wx'y' + xz$ is the
unique minimal expression.

Example: Two irredundant expressions for $f(w,x,y,z) = \sum(0,4,5,7,8,9,13,15)$

The Map Method

Example: $f(w,x,y,z) = \sum(1,5,6,7,11,12,13,15)$

- Only one irredundant form: f = wxy' + wyz + w'xy + w'y'z

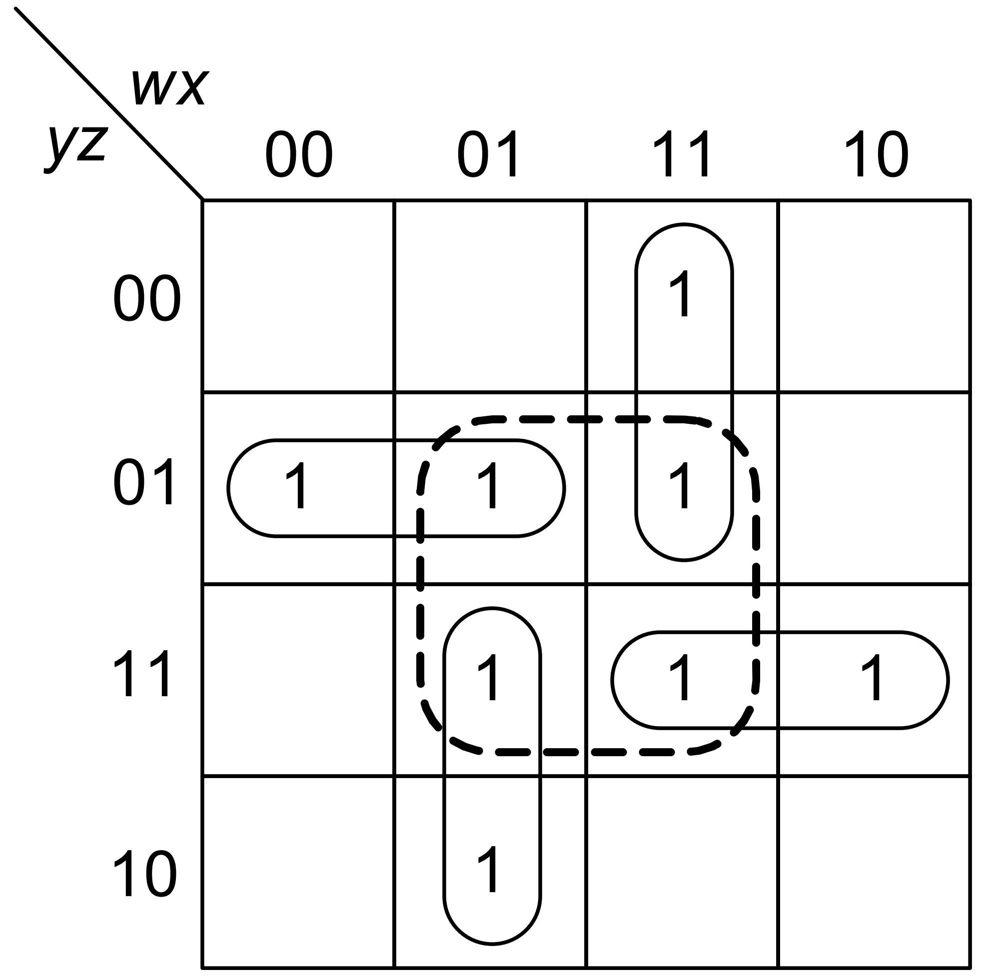

The Map Method: Earth is not Flat

A \ BC	00	01	11	10
0	000	001	011	010
1	100	101	111	110

A \ BC	00	01	11	10
0	1			1
1				

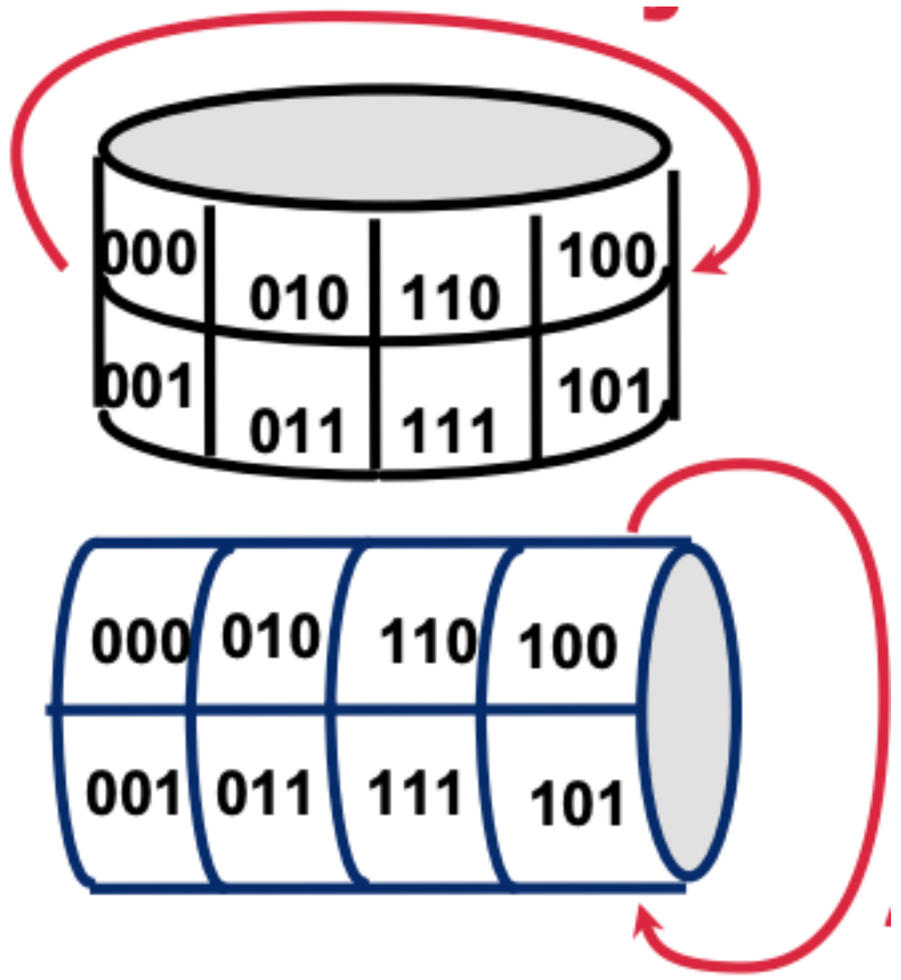

Minimal Product-of-Sums

- **Dual procedure**: product of a minimum number of sum factors, provided there is no other such product with the same number of factors and fewer literals
    - **<u>Variable corresponding to a 1 (0) is complemented (uncomplemented)</u>**
    - Cubes are formed of 0 cells
- **Example**: either one of minimal sum-of-products or minimal product-of-sums can be better than the other in literal count

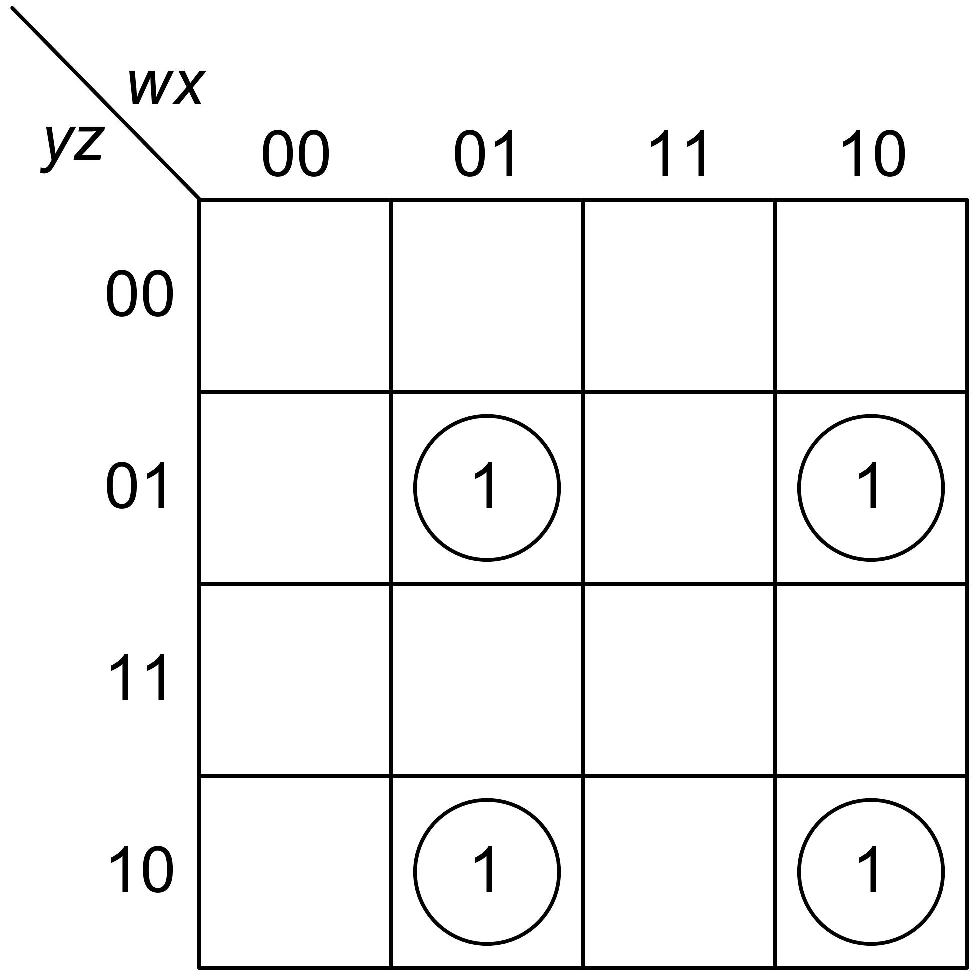

(a) Map of $f(x,y,z) = \sum(5,6,9,10)$
$= w'xy'z + wx'y'z + w'xyz' + wx'yz'$.

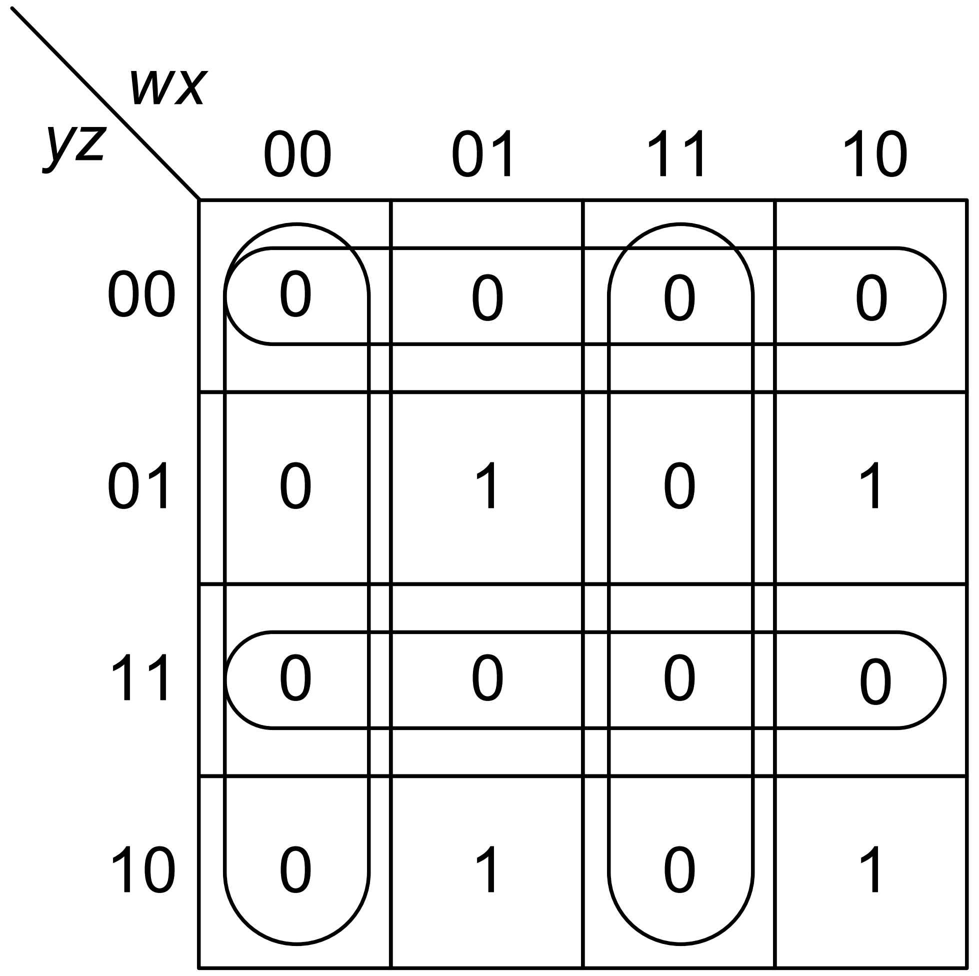

(b) Map of $f(x,y,z)$
$= \prod(0,1,2,3,4,7,8,11,12,13,14,15)$
$= (y + z)(y' + z')(w + x)(w' + x')$.

Let’s Try it..

- Implement **complement of** $f(A, B, C, D) = \prod(7,9,13)$.

Let's Try it..

- Implement $f(A, B, C, D) = \sum (0,2,8,12,13)$ with minimum number of gates.